

## EE 432/537 Power Electronics

### Laboratory Exercise #1

#### Objectives:

Become familiar with equipment

Examine two basic power electronic circuits


Explore PWM

#### Assignment 1

The concept of Pulse Width Modulation is widely used in Power Electronics. In a simple dc-dc converter the switch is turned on and off at a constant frequency  $f$ . The on time  $T_{on}$  is variable. The duty cycle or duty ratio  $D=T_{on}/T$ , where  $T=1/f$  is the period. In dc-ac inverters  $D$  is modulated to generate specific output waveshapes.

The low power control signal used to turn the switch on/off can be generated by an analog circuit or a microprocessor.

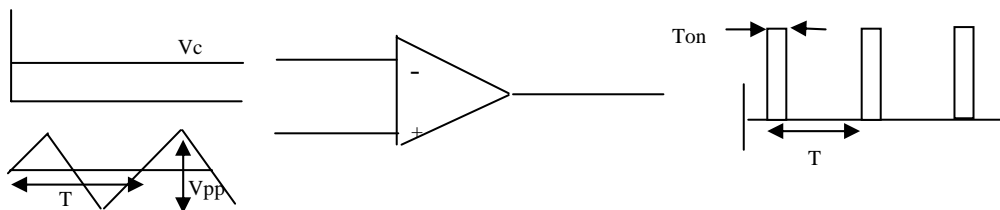The simplest analog PWM generator compares a triangular (or saw tooth) wave with peak to peak voltage  $V_{pp}$  with a variable dc level  $V_c$  as shown below.



In this assignment you are asked to build such a PWM generator.

#### Equipment

Proto-board  
LM 311

#### Assignment


Show that  $D=(0.5V_{pp}-V_c)/V_{pp}$

Use a comparator to realize the above circuit. Verify that you can vary  $D$  from  $\sim 0$  to 1. Show actual waveforms for a  $D=0.75$

## Assignment 2
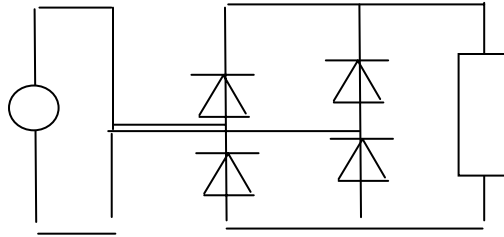
### Single Phase Rectifier

The single phase, full wave bridge rectifier circuit below converts ac to dc with ripple. In this assignment you are asked to build this circuit and verify its performance.



### Assignment

Use one phase of the 0-120V ac source and the diode bridge module connect single phase bridge rectifier. Use the isolator module and scope/DMM for measurements.

Derive a formula for the average dc voltage for a single phase bridge rectifier with resistive load.


Set the input voltage to 40 V rms. Obtain the waveform for output voltage and measure the average value (dc value). Check against your formula.

Turn everything off. Connect the electrolytic capacitor provided across the resistive load. Slowly bring up the ac voltage to 40 V (Why slowly?) Obtain the waveform for output voltage and measure the average value (dc value). Explain the waveform.

Verify lab measurements using TOPSPICE simulation. Your diode should be capable of handling at least 100 V.
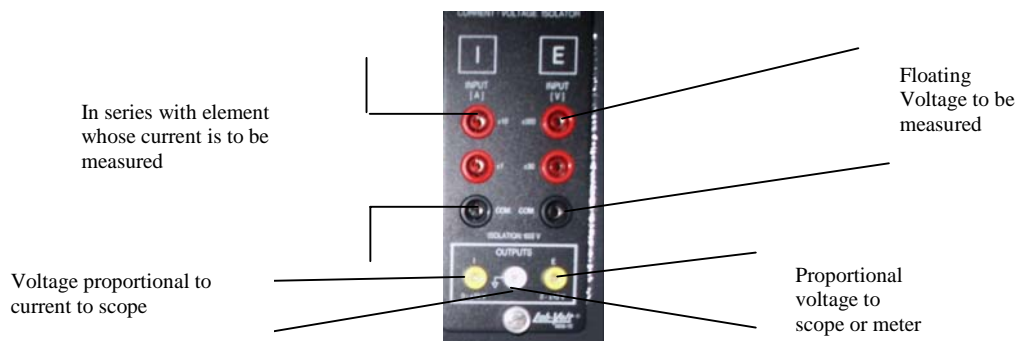
### Equipment:

LabVolt Bench ( 0-120V ac source)  
Power Diodes Module  
Voltage/Current Isolator Module  
DMM




# Assignment 3

## PWM dc-dc converter.

In homework problem 2.1 we looked at a PWM dc-dc converter. In this experiment we will look at such a converter.
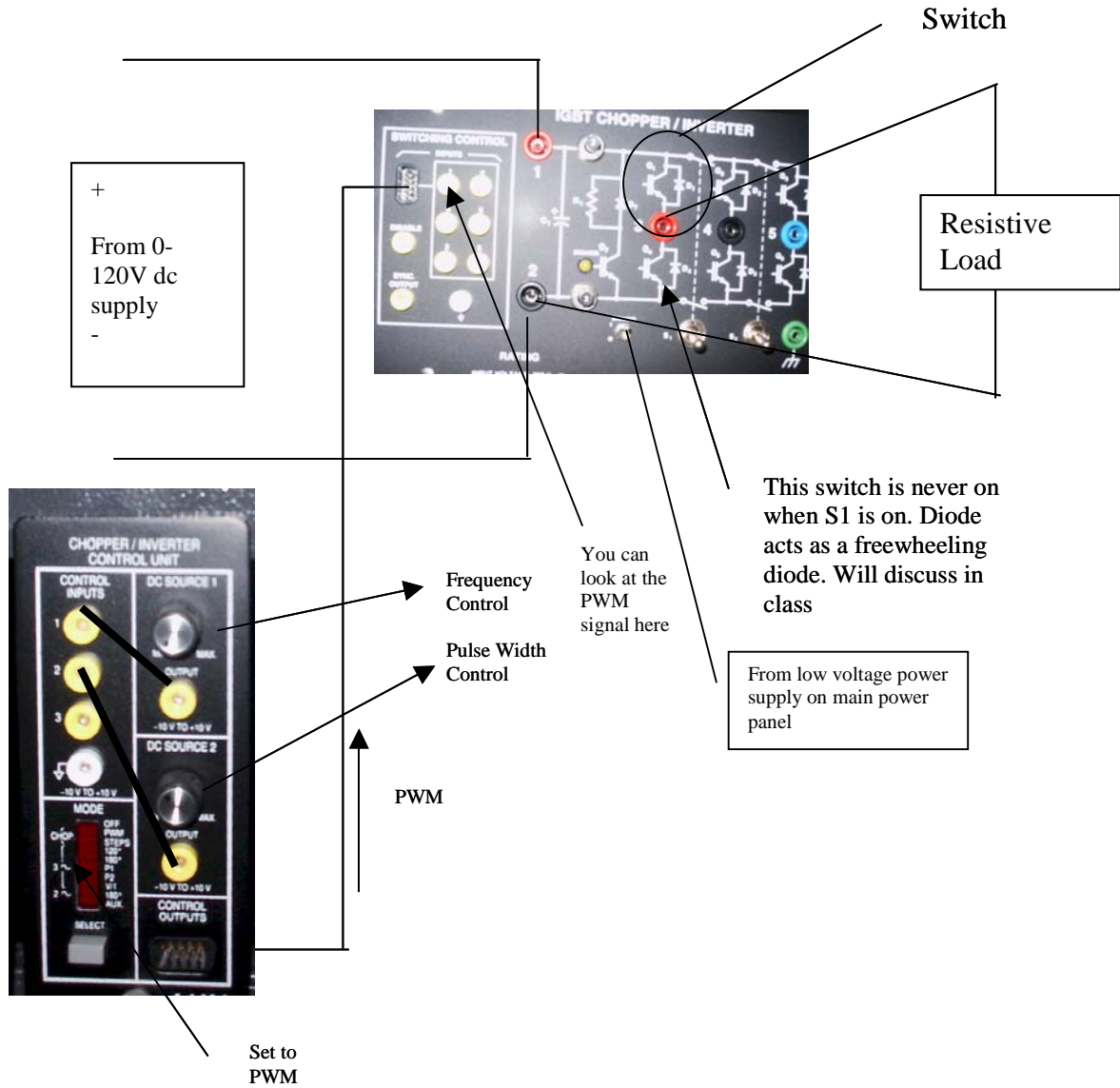
## Assignment

Implement the converter as suggested below. I know it looks clumsy since we use just one switch out of six. But trace the circuit out and make sure it matches Figure P2.1



Measure the average (dc ) output voltage for  $D= 0.2,0.5$  and  $0.8$ . Does the voltage vary linearly with  $D$ ?

Display the voltage across the IGBT and the PWM signal on a scope. Make a neat sketch. Do the waveforms make sense? Now display voltage across the IGBT and the current through the IGBT. Make a sketch and identify on and off regions.

Equipment:

LabVolt Bench (0-120V ac source)  
IGBT Chopper Inverter  
Resistive Load Box  
Voltage/Current Isolator Module  
DMM

Report

1. Maintain a lab or log book and record equipment used, ratings, circuit diagrams and observations. Record everything.
2. Turn in one report per group
  - a. Experiment Objectives
  - b. For each assignment
    - i. Objective
    - ii. Procedure
    - iii. Equipment
    - iv. Observations / Comparison with theory and simulation/  
Conclusions
3. Overall lessons learned.