

Balanced Three Phase Power Systems

Topics

Purpose

In balanced systems net instantaneous power is constant

Turbines driving a generator see constant counter torque corresponding to real power

Motors produce constant torque

Reactive power 'exists' in phases of the electric circuit but mechanical power is constant and corresponds to real power

Schematics, Nomenclature, Definitions

Wye – 3 and 4 wire

Delta

Conventions – Unless otherwise stated

Voltages are given Line-Line

Currents are line currents

Power is total three phase

Stuff is modeled as wye connected

Analysis -- Balanced Systems

Use per-phase model (also called single phase or line-neutral model)


Relationships between three phase voltages, currents and power

Instantaneous and Complex Power

Constant Power Loads

Problem Solving

Schematics, Nomenclature, Definitions

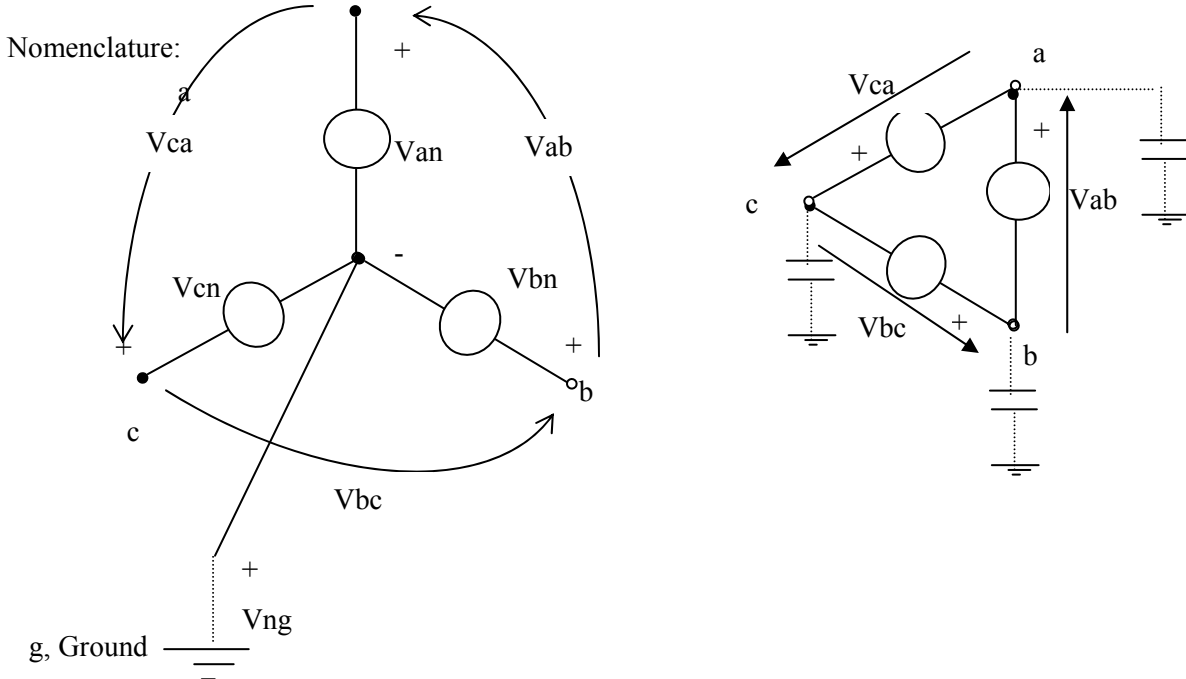

The source shown on the left, above, is a WYE connected source

a., b, c denote the three phase terminals

n is the neutral which may or may not be connected to ground g.

Ground g is typically the equipotential surface of earth with good contact achieved through driven ground rods, metal water pipes or more elaborate structures

Voltages V_{an} , V_{bn} and V_{cn} are LINE-NEUTRAL voltages

These are also popularly called PHASE voltages

Voltages V_{ab} , V_{bc} , V_{ca} are LINE-LINE voltages

Also called LINE voltages

Voltage V_{ng} is neutral to ground voltage

We can also define Voltages V_{ag} , V_{bg} , V_{cg} – these are line-ground voltages. Only V_{ag} is marked in the figure.

The source to the right is a DELTA connected source. It has no connection to ground except through stray capacitance. Only line-line voltages are defined.


Often, each leg in a delta is called a 'phase'

The voltage is also called a 'phase voltage'

BALANCED POSITIVE SEQUENCE VOLTAGE in a wye-connected source is defined as a set of three voltages, say line-neutral, with equal magnitudes and with phase b lagging phase a by 120deg and phase c lagging phase b by 120 deg.

$$V_{an} = VLN / \underline{0^\circ} \quad V_{bn} = VLN / \underline{-120^\circ} \quad V_{cn} = VLN / \underline{-240^\circ} \quad (\text{or } V_{cn} = VLN / \underline{-120^\circ})$$

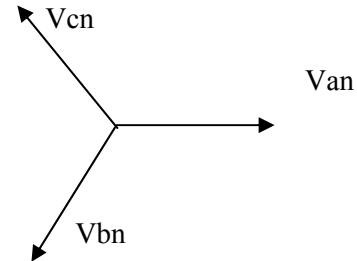These can be shown in a phasor diagram form




Balanced NEGATIVE Sequence voltages are defined as

$$V_{an} = VLN / \underline{0^\circ} \quad V_{bn} = VLN / \underline{+120^\circ} \quad V_{cn} = VLN / \underline{+240^\circ} \quad (\text{or } V_{cn} = VLN / \underline{+120^\circ})$$

These can be shown in a phasor diagram form.

BALANCED NEGATIVE SEQUENCE VOLTAGE in a wye-connected source is defined as a set of three voltages, say line-neutral,
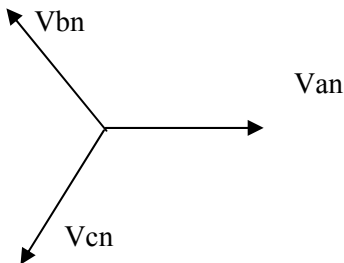
$$V_{an} = VLN / \underline{0^\circ} \quad V_{bn} = VLN / \underline{+120^\circ} \quad V_{cn} = VLN / \underline{+240^\circ} \quad (\text{or } V_{cn} = VLN / \underline{-120^\circ})$$



A positive sequence source can be turned into negative sequence by swapping a pair of leads

Sequence determines the direction of rotation of Polyphase ac motors

We will assume BPS unless otherwise stated


LINE-LINE and LINE –NEUTRAL VOLTAGES FOR BALANCED POSITIVE SEQUENCE

It is always true (think KVL) that $V_{ab} = V_{an} - V_{bn}$. In the case of a delta imagine 'n' to be a fictitious neutral point. Similarly, $V_{bc} = V_{bn} - V_{cn}$ and $V_{ca} = V_{cn} - V_{an}$.

We can then show that for BPS



$$V_{ab} = \sqrt{3} V_{an} / 30^\circ, V_{bc} = \sqrt{3} V_{bn} / 30^\circ, V_{ca} = \sqrt{3} V_{cn} / 30^\circ$$

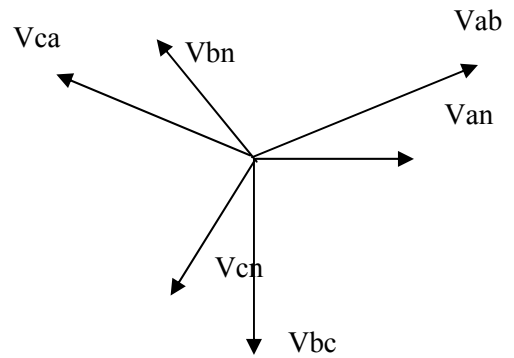The magnitude of L-L voltage $V_{LL} = V_{ab} = \sqrt{3} V_{LN}$



These relations apply to delta sources as well, with 'n' to be a fictitious neutral point. Thus a balanced delta source is equivalent to an ungrounded wye source.

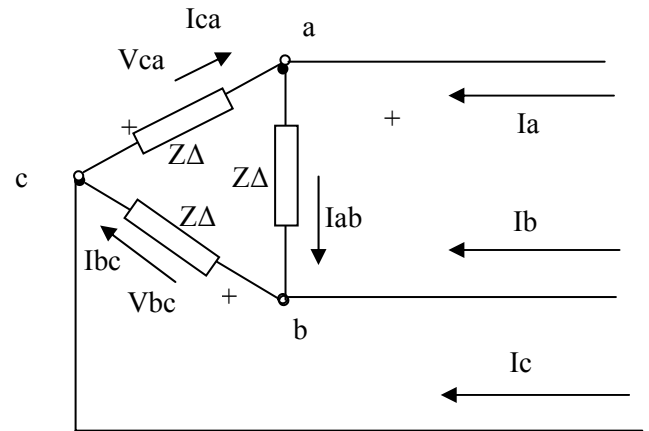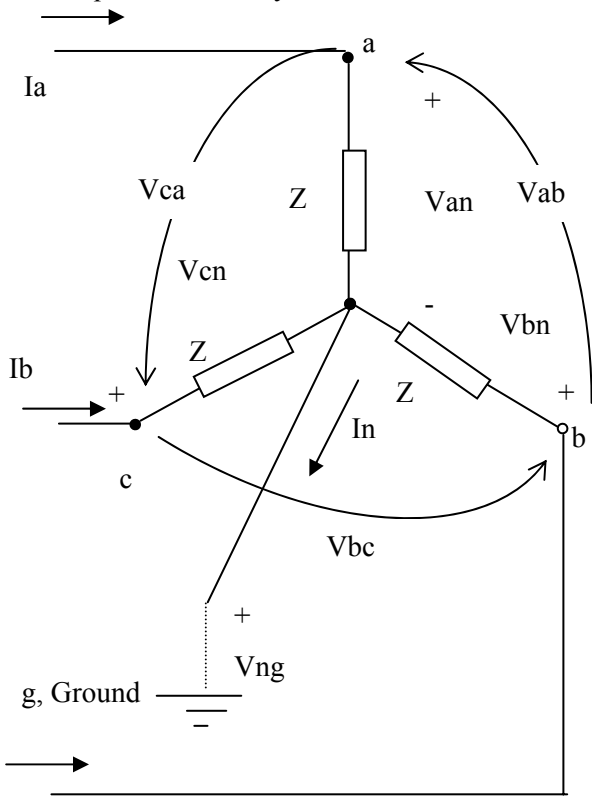BALANCED THREE PHASE LOADS consist of three equal impedances in a wye or delta connection. We will also model model three phase loads as constant KVA loads in which case the complex power S consumed in each phase will be assumed to be equal. Note that a delta-load is equivalent to a wye load with $Z_{\Delta} = 3Z$ and $S_{\Delta} = S$



Ic

THREE PHASE CURRENTS

In the loads above the wires connecting to the load terminals are the LINES

I_a, I_b, I_c are called LINE CURRENTS

-They are called phase currents for wye

I_n is called the neutral current Note: $I_n = I_a + I_b + I_c$

I_{ab}, I_{bc}, I_{ca} in the Delta load are delta currents

--These are often called phase currents for a delta

BLANCED POSITIVE SEQUENCE CURRENTS are defined as

$$I_a = I_L \angle 0^\circ \quad I_b = I_L \angle -120^\circ \quad I_c = I_L \angle -240^\circ$$

Can show that for a delta **load** $I_{ab} = (I_a / \sqrt{3}) \angle 30^\circ$, $I_{bc} = (I_b / \sqrt{3}) \angle 30^\circ$, $I_{ca} = (I_c / \sqrt{3}) \angle 30^\circ$ for BPS


BLANCED 3 PHASE SYSTEMS ANALYSIS


We need only consider wye connections since balanced delta sources and loads can be converted to wye

A balanced, positive sequence, 60 Hz, three-phase source supplies a balanced wye connected load through a three-phase transmission line. The neutral of the source is connected to that of the load through a wire with negligible impedance. The load impedance is 10 ohm/phase and line impedance is $1 + j1$ ohms per phase.

Find all line currents, line-neutral load voltages, line-line load voltages.

One line diagram

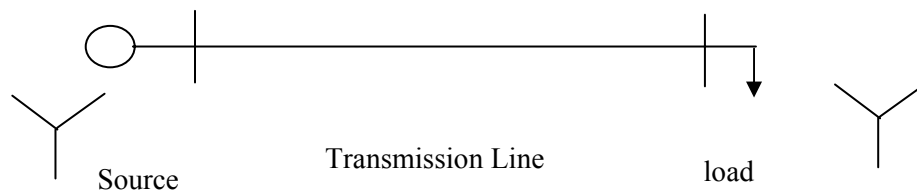

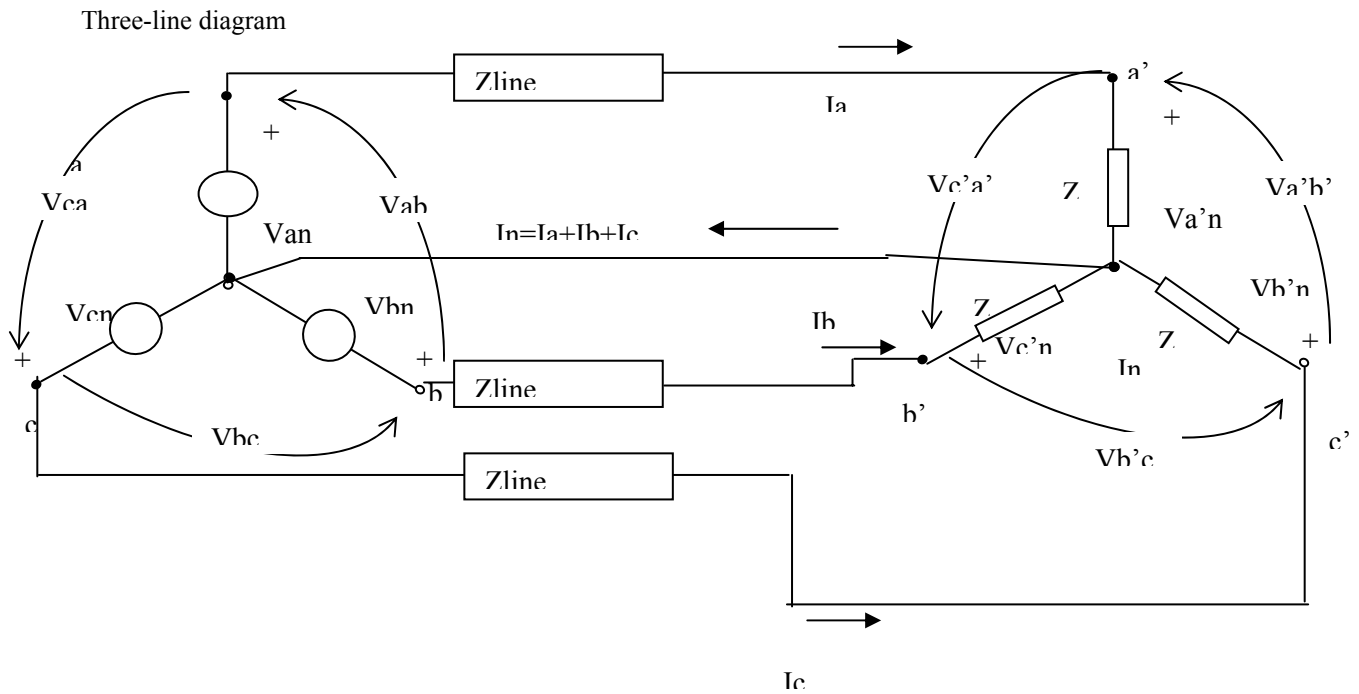

Remember, by convention, the given source voltage of 208 V is a LINE-LINE, RMS voltage

So $V_{ab} := 208 \cdot e^{j \cdot 0 \text{deg}}$

Since source is BPS

$V_{ab} := 208 \cdot e^{j \cdot 0 \text{deg}}$ $V_{bc} := 208 \cdot e^{j \cdot -120 \text{deg}}$ $V_{ca} := 208 \cdot e^{j \cdot 120 \text{deg}}$

Then $V_{an} := \frac{208}{\sqrt{3}} \cdot e^{j \cdot -30 \text{deg}}$ $V_{bn} := \frac{208}{\sqrt{3}} \cdot e^{j \cdot -150 \text{deg}}$ $V_{cn} := \frac{208}{\sqrt{3}} \cdot e^{j \cdot 90 \text{deg}}$ V

It is however convenient to let V_{an} be the voltage reference so let

$V_{ab} := 208 \cdot e^{j \cdot 30 \text{deg}}$ $V_{bc} := 208 \cdot e^{j \cdot -90 \text{deg}}$ $V_{ca} := 208 \cdot e^{j \cdot 150 \text{deg}}$

Then $V_{an} := \frac{208}{\sqrt{3}} \cdot e^{j \cdot 0 \text{deg}}$ $V_{bn} := \frac{208}{\sqrt{3}} \cdot e^{j \cdot -120 \text{deg}}$ $V_{cn} := \frac{208}{\sqrt{3}} \cdot e^{j \cdot 120 \text{deg}}$

Mesh analysis of the loop consisting of the phase source, line, load and neutral gives

$V_{an} = I_a Z_{line} + I_a Z$

$$Z_{line} := 1 + j \quad Z := 10$$

$$I_a := \frac{V_{an}}{Z + Z_{line}} \quad I_a = 10.828 - 0.984i \quad |I_a| = 10.872 \quad \arg(I_a) = -5.194 \text{ deg}$$

$$V_{a'n} := V_{an} - I_a \cdot Z_{line} \quad |V_{a'n}| = 108.723 \quad \arg(V_{a'n}) = -5.194 \text{ deg}$$

Similarly

$$I_b := \frac{V_{bn}}{Z + Z_{line}} \quad I_b = 10.828 - 0.984i \quad |I_b| = 10.872 \quad \arg(I_b) = -5.194 \text{ deg}$$

$$V_{b'n} := V_{bn} - I_b \cdot Z_{line} \quad |V_{b'n}| = 108.723 \quad \arg(V_{b'n}) = -125.194 \text{ deg}$$

$$I_c := \frac{V_{cn}}{Z + Z_{line}} \quad I_c = -4.561 + 9.869i \quad |I_c| = 10.872 \quad \arg(I_c) = 114.806 \text{ deg}$$

$$V_{c'n} := V_{cn} - I_c \cdot Z_{line} \quad |V_{c'n}| = 108.723 \quad \arg(V_{c'n}) = 114.806 \text{ deg}$$

Notice that load current and voltage are Balanced Positive Sequence!!!!

If sources, loads and network component are balance all voltages and currents are balanced

Therefore we could simply analyze phase 'a' and then find other voltages and currents by using the basic property of balanced voltages and currents.

BALANCED, THREE PHASE SYSTEMS ARE ANALYZED USING A PER PHASE OR LINE_NEUTRAL MODEL!!!!!!!!!!

Finally, note that, since I_a, I_b, I_c are balanced, $I_n = I_a + I_b + I_c = 0$; our conclusion thus holds even if the neutrals are not connected together.

GENERAL ANALYSIS AND UNBALANCED SYSTEMS

In the general case one would simply write KVL and KCL to solve the problem. In our example assume that the neutrals are not connected but that the circuit is balanced.

$$V_{an} - V_{bn} = V_{ab} = I_a Z_{line} + I_a Z_{load} - I_b Z_{load} - I_b Z_{line}$$

$$V_{bn} - V_{cn} = V_{bc} = I_b Z_{line} + I_b Z_{load} - I_c Z_{load} - I_c Z_{line}$$

$$V_{cn} - V_{an} = V_{ca} = I_c Z_{line} + I_c Z_{load} - I_a Z_{load} - I_a Z_{line}$$

Unfortunately, these equations are dependent so we need one more independent equation. KCL at the neutral (remember, neutrals are disconnected for this example)

$$I_a + I_b + I_c = 0$$

So, we have

$$V_{ab} = 208/\underline{30} = I_a(Z_{line} + Z_{load}) + I_b(-Z_{line} - Z_{load}) + I_c \cdot 0$$

$$V_{bc} = 208/\underline{-90} = I_c \cdot 0 + I_b(Z_{line} + Z_{load}) + I_c(-Z_{line} - Z_{load})$$

$$0 = I_a + I_b + I_c$$

In matrix form

$$V = ZI$$

$$V := \begin{pmatrix} 208 \cdot e^{j \cdot 30 \text{deg}} \\ 208 \cdot e^{j \cdot -90 \text{deg}} \\ 0 \end{pmatrix} \quad Z := \begin{pmatrix} 11 + j & -11 - j & 0 \\ 0 & 11 + j & -11 - j \\ 1 & 1 & 1 \end{pmatrix}$$

and I is the column vector of currents I_a , I_b , and I_c


$$\text{Then} \quad I := Z^{-1} \cdot V \quad I = \begin{pmatrix} 10.828 - 0.984i \\ -6.266 - 8.885i \\ -4.561 + 9.869i \end{pmatrix}$$

ANALYSIS of BALANCED SYSTEMS USING PER PHASE OR LINE_NEUTRAL MODEL


A balanced, positive sequence, 60 Hz, three-phase source supplies a balanced wye connected load through a three-phase transmission line. The neutral of the source is connected to that of the load through a wire with negligible impedance. The load impedance is 10 ohm/phase and line impedance is $1+j1$ ohms per phase.

Find all line currents, line-neutral load voltages, line-line load voltages.

One line diagram

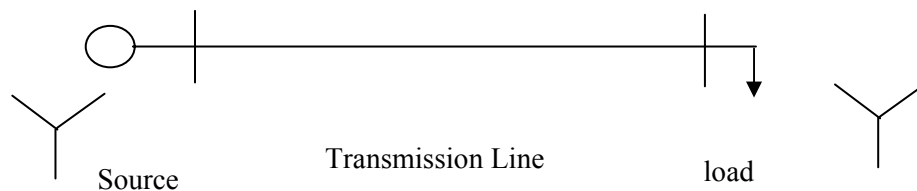

Per Phase Model or Line-neutral model

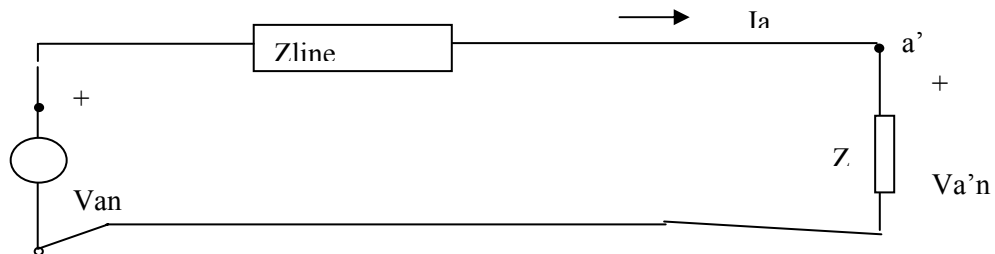

The model is valid whether or not the neutrals are tied, provided that the system is balanced

$$I_a := \frac{V_{an}}{Z + Z_{line}} \quad I_a = 10.828 - 0.984i \quad |I_a| = 10.872 \quad \arg(I_a) = -5.194 \text{ deg}$$

$$V_{a'n} := V_{an} - I_a \cdot Z_{line} \quad |V_{a'n}| = 108.723 \quad \arg(V_{a'n}) = -5.194 \text{ deg}$$

$$I_b := I_a \cdot e^{j-120\text{deg}} \quad V_{b'n} := V_{a'n} \cdot e^{j-120\text{deg}}$$

$$I_c := I_b \cdot e^{j-120\text{deg}} \quad V_{c'n} := V_{b'n} \cdot e^{j-120\text{deg}}$$

$$|I_b| = 10.872 \quad \arg(I_b) = -125.194 \text{ deg} \quad |V_{b'n}| = 120.089 \quad \arg(V_{b'n}) = -120 \text{ deg}$$

$$|I_c| = 10.872 \quad \arg(I_c) = 114.806 \text{ deg} \quad |V_{c'n}| = 120.089 \quad \arg(V_{c'n}) = 120 \text{ deg}$$


INSTANTANEOUS AND COMPLEX POWER

See Section 2.6


- The instantaneous power in each phase has oscillating components
- The total instantaneous power is constant
- The average power in each phase is REAL POWER per phase
 - o $P_{1\phi} = V_{an} I_a \cos \phi$; where $\phi = \theta_{V_{an}} - \theta_{I_{an}}$
- The REACTIVE POWER per phase is
 - o $Q_{1\phi} = V_{an} I_a \sin \phi$; where $\phi = \theta_{V_{an}} - \theta_{I_{an}}$
- The COMPLEX POWER per phase is
 - o $S_{1\phi} = V_{an} I_a^* = P_{1\phi} + j Q_{1\phi}$
- The total 3 phase complex power is defined as $S_{3\phi} = 3 S_{1\phi} = 3 V_{an} I_a^*$
- Useful cook book formulas $|S_{3\phi}|$
 - o $P = \sqrt{3} V_{LL} I_L \cos \phi$ where $\phi = \theta_{V_{an}} - \theta_{I_{an}}$, V_{LL} is l-l voltage magnitude and I_L is line current magnitude
 - o $|S| = |S_{3\phi}| = \sqrt{3} V_{LL} I_L$

Continuing the example from the last lecture

One line diagram

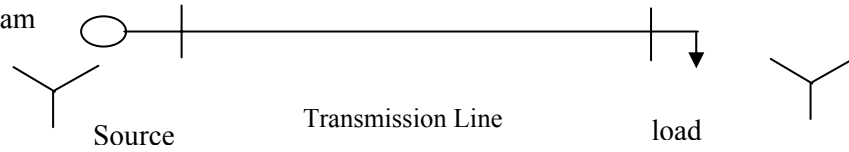

Per Phase Model or Line-neutral model

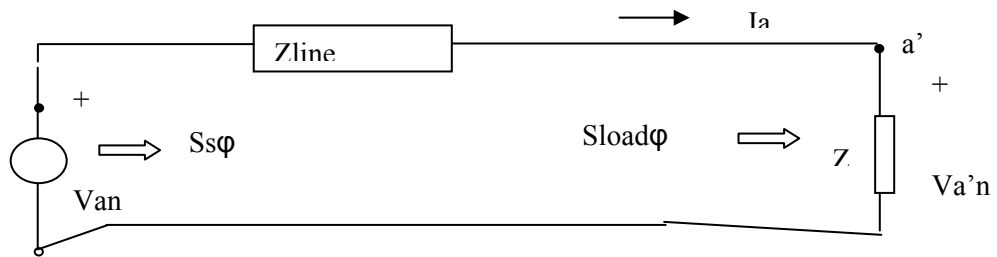

Remember, by convention, the given source voltage of 208 V is a LINE-LINE, RMS voltage

It is convenient to let V_{an} be the voltage reference so let

Then $V_{an} := \frac{208}{\sqrt{3}} \cdot e^{j \cdot 0 \text{deg}}$ V

$Z_{line} := 1 + j$ $Z := 10$ ohm

$I_a := \frac{V_{an}}{Z + Z_{line}}$ $I_a = 10.828 - 0.984i$ $|I_a| = 10.872$ $\arg(I_a) = -5.194 \text{deg}$ A

$V_{a'n} := V_{an} - I_a \cdot Z_{line}$ $|V_{a'n}| = 108.723$ $\arg(V_{a'n}) = -5.194 \text{deg}$ V

Complex power

Delivered to Load	$S_{load\phi} := V_{a'n} \cdot \bar{I}_a$	$S_{load\phi} = 1.182 \times 10^3$	$\frac{VA}{\text{phase}}$
	$S_{load3\phi} := 3 \cdot V_{a'n} \cdot \bar{I}_a$	$S_{load3\phi} = 3.546 \times 10^3$	VA Total or Three-phase (Default)
Delivered by Source	$S_{s\phi} := 3 \cdot V_{an} \cdot \bar{I}_a$	$S_{s\phi} = 3.901 \times 10^3 + 354.623i$	$\frac{VA}{\text{phase}}$
	$S_{s3\phi} := 3 \cdot V_{an} \cdot \bar{I}_a$	$S_{s3\phi} = 3.901 \times 10^3 + 354.623i$	VA
Loss	$S_{loss3\phi} := S_{s3\phi} - S_{load3\phi}$	$S_{loss3\phi} = 354.623 + 354.623i$	VA


From this point on we will drop the 3φ subscript on total 3 phase power.

PROBLEM SOLVING

Example 1 Three Phase Systems **Constant KVA load**

A three phase, 60 Hz, positive sequence source supplies a 39KVA, 0.9 pf lagging load through a transmission line of impedance 0.1+j0.1 ohm per phase. Determine the source voltage needed to obtain 208 V at the load. Also calculate the complex power supplied by the source.

Per phase or Line-Neutral model

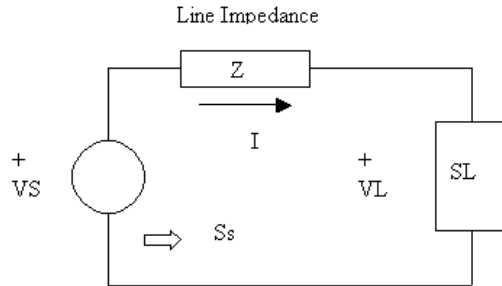

Line Impedance $z := 0.1 + j \cdot 0.1$ ohm per phase

Load complex power $SL := 39000 e^{j \cdot \text{acos}(.9)}$ Total or three phase
 $SL\phi := \frac{SL}{3}$ $SL\phi = 1.17 \times 10^4 + 5.667i \times 10^3$ VA per phase

Load Voltage $VLL := 208$ V LL
 $VL := \left(\frac{VLL}{\sqrt{3}}\right) \cdot e^{j \cdot 0}$ V line-neutral

So Line Current $IL := \left(\frac{SL\phi}{VL}\right)$ $IL = 97.428 - 47.186i$ $|IL| = 108.253$ $\arg(IL) = -25.842\text{deg}$

Then $VS := VL + z \cdot IL$ $|VS| = 134.644$ $\arg(VS) = 2.138\text{deg}$

This answer is in line to neutral volts.

So magnitude of source vltage in line-line $134.644\sqrt{3} = 233.21$ V

Load Power $SL = 3.51 \times 10^4 + 1.7i \times 10^4$ VA Given, Three phase

Source Power $SS := 3 \cdot VS \cdot \overline{IL}$ $SS = 3.862 \times 10^4 + 2.052i \times 10^4$ VA Three phase

Loss $Loss := SS - SL$ $Loss = 3.516 \times 10^3 + 3.516i \times 10^3$ VA

Can calculate Loss as follows

$$Loss := (|IL|)^2 \cdot z \cdot 3 \quad Loss = 3.516 \times 10^3 + 3.516i \times 10^3 \quad VA$$

Source power factor $pfs := \cos(\arg(VS) - \arg(IL))$ $pfs = 0.883$ lag


AN Aside

Cokbook approach to calculating load current

$$IL := \left(\frac{|SL|}{\sqrt{3} \cdot VLL}\right) \cdot e^{j \cdot -\text{acos}(0.9)} \quad |IL| = 108.253 \quad \arg(IL) = -25.842\text{deg}$$

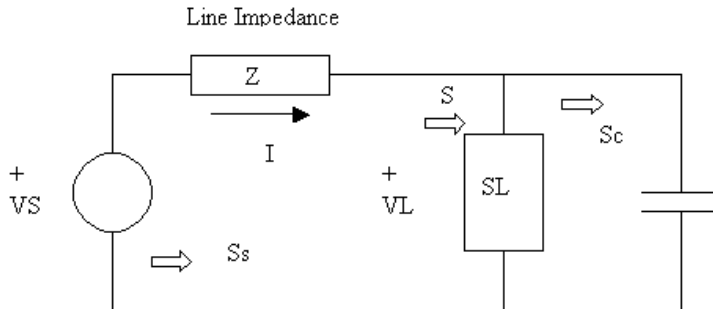Example 2: Power Factor correction

For the system in the previous example, correct the power factor to unity. Determine capacitor required, source voltage, and loss. Load voltage should be 208 V



Unless otherwise noted all powers are three phase, voltages are line-line, currents are line currents

Let Qc represent the reactive power SUPPLIED by the capacitor

Complex power delivered TO Capacitor is SC = -j QC

Let S represent load complex power after correction.

$$S = S_L + S_C = P_L + j Q_L - j Q_C$$

Let ϕ_{old} represent the original power factor angle and ϕ_{new} the desired one.

$$\text{Then } \tan(\phi_{old}) = Q_L/P_L \text{ and } \tan(\phi_{new}) = (Q_L - Q_C)/P_L$$

Note the real power must remain the same, while reactive power changes

$$\text{Thus } (Q_L - Q_C)/Q_L = \tan(\phi_{new})/\tan(\phi_{old}) \text{ so } Q_C = Q_L - P_L \tan(\phi_{new})$$

In our case the desired power factor is 1, so $\phi_{new} = 0$. Solve for QC

$$S_L = 3.51 \times 10^4 + 1.7i \times 10^4 \text{ VA} \quad P_L := \text{Re}(S_L) \quad Q_L := \text{Im}(S_L)$$

$$\phi_{new} := 0$$

$$Q_C := Q_L - P_L \tan(\phi_{new}) \quad Q_C = 1.7 \times 10^4 \text{ VAR}$$

After Correction

$$S_C := -j \cdot Q_C \quad S := S_L + S_C \quad \text{VA Three phase}$$

$$S_\phi := \frac{S}{3} \quad S_\phi = 1.17 \times 10^4 \text{ VA per phase}$$

$$\text{At load} \quad V_{LL} := 208 \text{ (line - line)V}$$

$$V_L := \frac{V_{LL}}{\sqrt{3}} \quad \text{use this as phasor reference}$$

$$\text{So } I_L := \left(\frac{S_\phi}{V_L} \right) \quad I_L = 97.428 \quad |I_L| = 97.428 \quad \arg(I_L) = 0 \text{ deg}$$

$$\text{Then } V_S := V_L + z I_L \quad |V_S| = 130.197 \quad \arg(V_S) = 4.292 \text{ deg}$$

$$\text{Source voltage needed} \quad 130.197\sqrt{3} = 225.508 \quad V_{L-1}$$

Note improvement in voltage, current and loss

$$\begin{array}{ll}
 \text{Load Power} & S_L = 3.51 \times 10^4 + 1.7i \times 10^4 \\
 \text{Source Power} & \underline{S_S} := 3V_S \cdot \overline{I_L} \quad S_S = 3.795 \times 10^4 + 2.848i \times 10^3 \\
 \text{Loss} & \underline{Loss} := S_S - S \quad \text{Loss} = 2.848 \times 10^3 + 2.848i \times 10^3
 \end{array}$$

Example 3

- Assume that the capacitor is wye connected; calculate the capacitance per phase
 - Assume that the capacitor is delta connected; calculate the capacitance per phase
- Calculate the phasor line currents I_a, I_b, I_c
 Calculate the phasor delta currents I_{ab}, I_{bc}, I_{ca}

$$\text{So} \quad I_C := \left(\frac{\frac{S_C}{3}}{\frac{V_L}{\sqrt{3}}} \right) \quad I_C = 81.729i$$

For wye

$$\text{Then} \quad Z_C := \frac{V_L}{I_C} \quad Z_C = -1.469i \quad \text{ohm}$$

$$X_C := -\text{Im}(Z_C) \quad X_C = 1.469$$



$$\text{Since } X_C = 1/\omega C \quad \underline{C} := \frac{1}{377 \cdot X_C} \quad C = 1.805 \times 10^{-3}$$

$$\text{For delta} \quad \underline{Z_C} := 3 \cdot Z_C$$

$$Z_C = -4.408i \quad \text{ohm} \quad \underline{X_C} := -\text{Im}(Z_C)$$

$$X_C = 4.408 \quad \underline{C} := \frac{1}{377 \cdot X_C} \quad C = 6.017 \times 10^{-4}$$

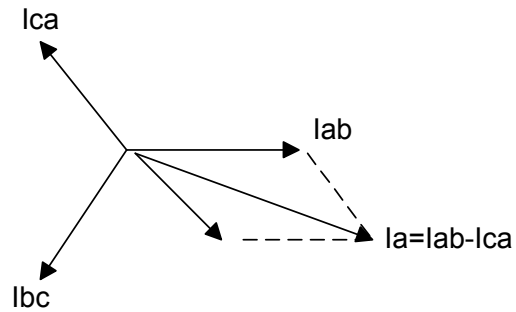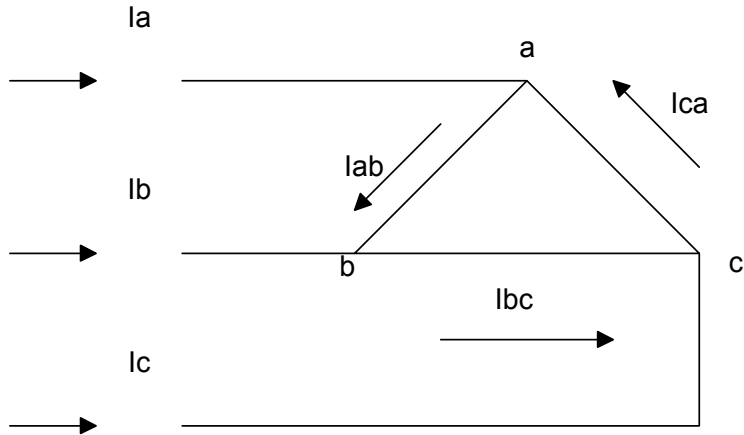Note, compared to the wye connection I need less capacitance per phase but the capacitors must be designed for 208 rather than 120 V



$$I_a := 6.287i$$

$$I_b := I_a \cdot e^{i \cdot -120\text{deg}}$$

$$I_c := I_a \cdot e^{i \cdot 120\text{deg}}$$

$$I_{ab} := \left(\frac{1}{\sqrt{3}} \cdot I_a \cdot e^{i \cdot 30\text{deg}} \right)$$

$$I_{bc} := \frac{1}{\sqrt{3}} \cdot I_b \cdot e^{i \cdot 30\text{deg}}$$

$$I_{ca} := \frac{1}{\sqrt{3}} \cdot I_c \cdot e^{i \cdot 30\text{deg}}$$

Corrected

$$|I_{ab}| = 3.63 \quad \arg(I_{ab}) = 120\text{deg}$$

$$|I_{bc}| = 3.63 \quad \arg(I_{bc}) = 7.01 \times 10^{-15} \text{deg}$$

$$|I_{ca}| = 3.63 \quad \arg(I_{ca}) = -120\text{deg}$$