

EE431 Fall 2008

Report Due Oct. 21 2008

Transmission Line Design Project – Assignment 2


Extend your design tool to:

1. Perform a full-load and no load analysis and display
  - a. At Full load: Sending end voltage, Sending end complex power, Real Power Loss and Reactive power Loss
  - b. At No load (Assuming a sending end voltage equal to that in Part 1): Receiving end voltage, Sending end complex power, Real Power Loss and Reactive power Loss
  - c. Voltage Regulation
  - d. Loadability at nominal voltage for  $\delta=35$  deg

Use data from homework problems and verify your tool via hand calculations.

What to turn in:

500 KV

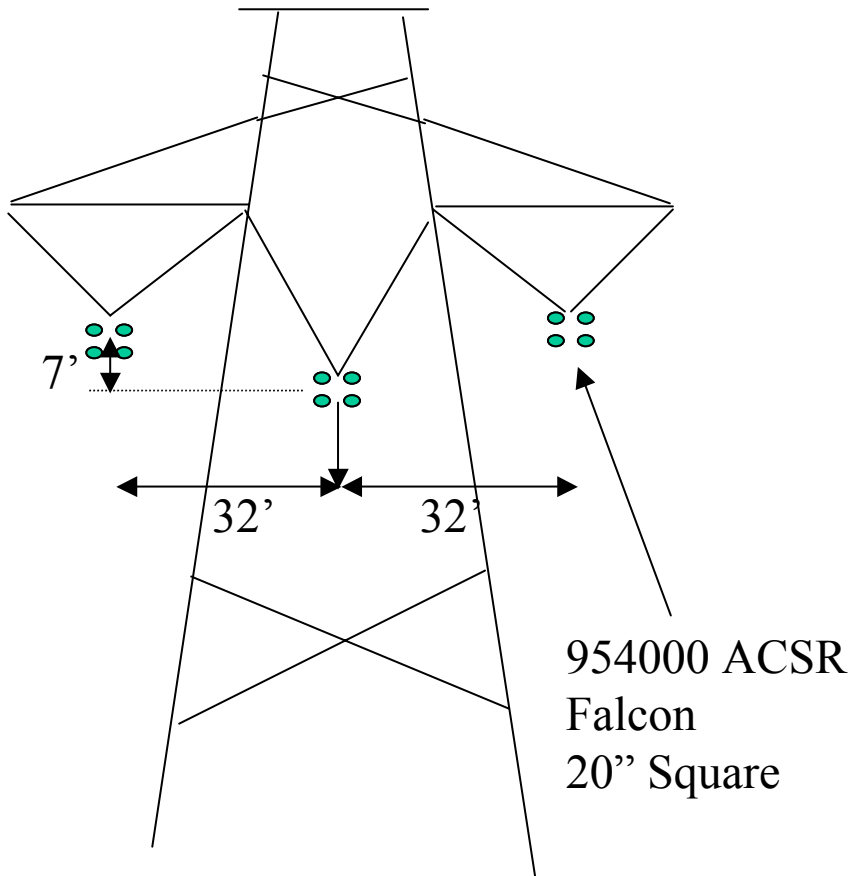

For the 200 mile long line shown

Find  $z$  and  $y$

Calculate ABCD parameters based on long line model

The receiving end load is 600 MW at 0.95 power factor lag

Calculate Voltage regulation

Power loss at full load

Sending end power at full load and no load

Loadability for  $\delta=35$  deg

### Step 1 Conductor Parameters

$$\text{Conductor Resistance} \quad \underline{R} := 0.0684 \quad \frac{\text{ohm}}{\text{mi}}$$

$$\text{GMR} \quad r' := 0.052 \quad \text{ft}$$

$$\text{Bundle spacing} \quad d := 20 \quad \text{in} \quad \underline{d} := \frac{20}{12} \quad d = 1.667 \quad \text{ft}$$

### Phase Distances

$$D_{12} := \sqrt{32^2 + 7^2} \quad D_{12} = 32.757 \quad \text{ft} \quad D_{23} := D_{12} \quad \text{ft} \quad D_{13} := 64 \quad \text{ft}$$

### Step 2 Line Resistance Per Phase

$$\underline{R} := \frac{R}{4} \quad R = 0.017 \quad \frac{\text{ohm}}{\text{mi}}$$

### Step 3 Bundle GMR

$$D_{sL} := \sqrt[4]{r' \cdot d \cdot d \cdot \sqrt{2} d}$$

$$D_{sL} = 0.764 \quad \text{ft}$$

### Step 2 GMD

$$D_{eq} := \sqrt[3]{D_{12} \cdot D_{23} \cdot D_{13}} \quad \text{ft}$$

$$D_{eq} = 40.951$$

### Step 5 impedance

In ohm/mi at 60 Hz

$$X := 0.1213 \cdot \ln\left(\frac{D_{eq}}{D_{sL}}\right) \quad X = 0.483 \quad \frac{\text{ohm}}{\text{mi}} \quad \text{per phase}$$

Impedance  $z := R + i \cdot X \quad z = 0.017 + 0.483i \quad \frac{\Omega}{\text{mi}}$

Capacitance

Outer diameter  $od := 1.545 \text{ "}$

Radius ( not GMR)  $r := \frac{od}{24} \text{ feet}$

$D_{sc} := \sqrt[4]{r \cdot d \cdot d \cdot \sqrt{2} d} \quad D_{sc} = 0.806 \text{ ft}$

Capacitance

$C := 2 \cdot \pi \cdot 8.854 \cdot \frac{10^{-12}}{\ln\left(\frac{D_{eq}}{D_{sc}}\right)} \quad C = 1.416 \times 10^{-11} \quad \frac{F}{m}$

Shunt susceptance

$B_c := 2 \cdot \pi \cdot 8.854 \cdot 10^{-12} \cdot 1609 \cdot \frac{377}{\ln\left(\frac{D_{eq}}{D_{sc}}\right)} \quad B_c = 8.59 \times 10^{-6} \quad \frac{\text{mho}}{\text{mi}}$

$y := i \cdot B_c$

Long line

$$\gamma := \sqrt{z \cdot y} \quad Z_c := \sqrt{\frac{z}{y}} \quad \gamma = 3.605 \times 10^{-5} + 2.037i \times 10^{-3} \quad Z_c = 237.155 - 4.197i$$

$$l := 200 \\ \underline{\underline{A}} := \cosh(\gamma \cdot l) \quad B := Z_c \cdot \sinh(\gamma \cdot l) \quad \underline{\underline{C}} := \frac{\sinh(\gamma \cdot l)}{Z_c} \quad D := A$$

$$A = 0.918 + 2.857i \times 10^{-6} \quad B = 3.233 + 93.95i \quad C = -1.655 \times 10^{-6} + 1.671i \times 10^{-3}$$

$$B = 3.233 + 93.95i$$

Check  $A \cdot D - B \cdot C = 1$

$$Y' := \frac{2 \cdot \tanh\left(\gamma \cdot \frac{l}{2}\right)}{Z_c} \quad Z' := Z_c \cdot \sinh(\gamma \cdot l)$$

$$Y' = 8.699 \times 10^{-7} + 1.742i \times 10^{-3} \quad Z' = 3.233 + 93.95i$$

Performance of uncompensated line

Full and no load ABCD matrix

$$ABCDline := \begin{pmatrix} A & B \\ C & D \end{pmatrix} \quad ABCD := ABCDline$$

Full Load Conditions

Line Length  $l := 200$

Per phase Receiving end Complex power  $SR\phi := \left(\frac{1}{3}\right) \cdot \left(\frac{600000000}{0.95}\right) \cdot e^{i \cdot \text{acos}(0.95)} \text{ VA}$

Receiving end l-n voltage  $VR := \frac{500000}{\sqrt{3}} \text{ V}$

Receiving end(load) current( Overbar represents complex conjugate)

$$IR := \overline{\left(\frac{SR\phi}{VR}\right)} \quad |IR| = 729.285 \quad \arg(IR) = -18.195 \text{ deg}$$

$$VRfl := \frac{500000}{\sqrt{3}} \text{ V} \quad IRfl := IR \quad IR = 692.82 - 22.4719i$$

$$Vs := A \cdot VRfl + B \cdot IRfl \quad |Vs| = 2.96 \times 10^5 \text{ l-n} \quad \arg(Vs) = 12.723 \text{ deg}$$

$$Is := C \cdot VRfl + D \cdot IRfl \quad |Is| = 693.276 \quad \arg(Is) = 23.393 \text{ deg}$$

$$Vrnl := \frac{Vs}{A} \quad |Vrnl| = 3.223 \times 10^5 \text{ Vl-n}$$

$$\sqrt{3} \cdot |Vs| = 5.126 \times 10^5$$

$$SSfl := 3 \cdot Vs \cdot \overline{Is} \quad SSfl = 6.049 \times 10^8 - 1.14i \times 10^8 \quad \text{Sending end power}$$

$$\text{Losses} \quad Sloss := (Vs \cdot \overline{Is} - VRfl \cdot \overline{IRfl}) \cdot 3 \quad Sloss = 4.886 \times 10^6 - 3.112i \times 10^8$$

### No load analysis

$$V_{Rnl} := \frac{V_s}{A} \quad |V_{Rnl}| = 3.223 \times 10^5 \quad \sqrt{3} \cdot |V_{rnl}| = 5.583 \times 10^5$$

$$I_{snl} := C \cdot V_{Rnl} \quad |I_{snl}| = 538.586$$

### Voltage regulation

$$\text{Reg} := \frac{(|V_{Rnl}| - |V_{Rfl}|) \cdot (100)}{|V_{Rfl}|} \quad \text{Reg} = 11.658 \quad \text{percent}$$

### Step 3d Loadability at $\delta=35$ deg Remember, we use rated values for voltages

$$V_s := \frac{50000}{\sqrt{3}} \quad V_r := \frac{50000}{\sqrt{3}}$$

$$P_{\max} := \left[ |V_s| \cdot \frac{|V_r| \cdot \cos\left(\arg(B) - 90 \cdot \frac{3.14}{180}\right)}{|B|} - (|V_r|)^2 \cdot \text{Re}\left(\frac{A}{B}\right) \right] \cdot 3 \quad P_{\max} = 2.566 \times 10^7$$

$$P_{\max} := \left[ |V_s| \cdot \frac{|V_r| \cdot \cos\left(\arg(B) - 35 \cdot \frac{3.14}{180}\right)}{|B|} - (|V_r|)^2 \cdot \text{Re}\left(\frac{A}{B}\right) \right] \cdot 3 \quad P_{\max} = 1.507 \times 10^7$$