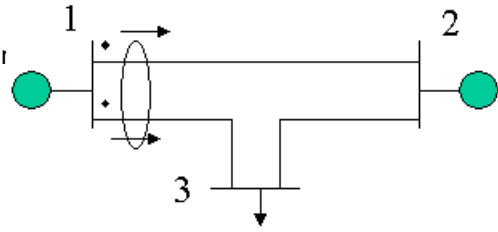


Consider the 3-bus System from Text page 54-55. We are assuming a balanced steady state and working with a per phase model Line impedances given are

For the mutually coupled lines from bus 1-2 and 1-3 let us assume that the primitive impedance matrix denoted by  $z_{1213}$  is

$$z_{1213} := \begin{pmatrix} .02 + .3i & .05i \\ .05i & .01 + .1i \end{pmatrix}$$

$$z_{23} := .01 + .1i$$



We will again ignore capacitance for simplicity and assume the following generator impedances

$$z_{g1} := .1i$$

$$z_{g2} := .1i$$

$z_{1213}$  was written in class as  $\begin{matrix} z_{12} & M \\ M & z_{13} \end{matrix}$

The primitive admittance matrix for just the coupled lines

$$y_{1213} := z_{1213}^{-1}$$

$y_{1213}$  was written as  $\begin{matrix} y_{12} & m \\ m & y_{13} \end{matrix}$

$$y_{1213} = \begin{pmatrix} 0.295 - 3.609i & -0.325 + 1.772i \\ -0.325 + 1.772i & 1.238 - 10.762i \end{pmatrix}$$

$$y_{\text{prim}} := \begin{pmatrix} y_{1213_{1,1}} & 0 & y_{1213_{1,2}} & 0 & 0 \\ 0 & \frac{1}{z_{23}} & 0 & 0 & 0 \\ y_{1213_{2,1}} & 0 & y_{1213_{2,2}} & 0 & 0 \\ 0 & 0 & 0 & \frac{1}{z_{g1}} & 0 \\ 0 & 0 & 0 & 0 & \frac{1}{z_{g2}} \end{pmatrix}$$

Since line currents are directed from bus 1 to 2 and bus 1 to 3 for this example

$$C := \begin{pmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \\ 1 & 0 & -1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{pmatrix}$$

$$Y := C^T \cdot y_{\text{prim}} \cdot C$$

$$Y = \begin{pmatrix} 0.884 - 20.827i & 0.03 + 1.837i & -0.914 + 8.99i \\ 0.03 + 1.837i & 1.285 - 23.51i & -1.315 + 11.673i \\ -0.914 + 8.99i & -1.315 + 11.673i & 2.229 - 20.663i \end{pmatrix}$$

The modified rules for Y are

If line from bus i to bus j is coupled to the line from bus k to bus l and the primitive admittance matrix is

$$Y := \begin{pmatrix} y1 & m \\ m & y2 \end{pmatrix}$$

Add y1 to Y<sub>ii</sub> term  
 Add y1 to Y<sub>jj</sub> term  
 Add y2 to Y<sub>kk</sub> term  
 Add y2 to Y<sub>ll</sub> term

Add -y1 to Y<sub>ij</sub> term  
 Add -y1 to Y<sub>ji</sub> term  
 Add -y2 to Y<sub>kl</sub> term  
 Add -y2 to Y<sub>lk</sub> term

The above are just the usual rules. In addition

Add m to Y<sub>ik</sub> term  
 Add m to Y<sub>ki</sub> term  
 Add m to Y<sub>jl</sub> term  
 Add m to Y<sub>lj</sub> term

Add -m to Y<sub>il</sub> term  
 Add -m to Y<sub>li</sub> term  
 Add -m to Y<sub>jk</sub> term  
 Add -m to Y<sub>kj</sub> term

So

$$Y := \begin{bmatrix} \left(\frac{1}{z_{g1}}\right) + y_{1213_{1,1}} + y_{1213_{2,2}} + y_{1213_{1,2}} + y_{1213_{1,2}} & -y_{1213_{1,1}} - y_{1213_{1,2}} & -y_{1213_{2,2}} - y_{1213_{1,2}} \\ -y_{1213_{1,1}} - y_{1213_{1,2}} & \left(\frac{1}{z_{g2}}\right) + y_{1213_{1,1}} + \left(\frac{1}{z_{23}}\right) & \left(\frac{-1}{z_{23}}\right) + y_{1213_{1,2}} \\ -y_{1213_{2,2}} - y_{1213_{1,2}} & \left(\frac{-1}{z_{23}}\right) + y_{1213_{1,2}} & \left(\frac{1}{z_{23}}\right) + y_{1213_{2,2}} \end{bmatrix}$$

$$Y = \begin{pmatrix} 0.884 - 20.827i & 0.03 + 1.837i & -0.914 + 8.99i \\ 0.03 + 1.837i & 1.285 - 23.51i & -1.315 + 11.673i \\ -0.914 + 8.99i & -1.315 + 11.673i & 2.229 - 20.663i \end{pmatrix}$$

Fault calculation example

$$Z := Y^{-1} \quad Z = \begin{pmatrix} 8.975 \times 10^{-4} + 0.071i & -8.975 \times 10^{-4} + 0.029i & -5.492 \times 10^{-6} + 0.047i \\ -8.975 \times 10^{-4} + 0.029i & 8.975 \times 10^{-4} + 0.071i & 5.492 \times 10^{-6} + 0.053i \\ -5.492 \times 10^{-6} + 0.047i & 5.492 \times 10^{-6} + 0.053i & 5.146 \times 10^{-3} + 0.098i \end{pmatrix}$$

Three phase fault at bus 3; prefault voltages = 1 pu

$$I_f := \frac{1}{Z_{3,3}} \quad I_f = 0.532 - 10.156i$$

$$V := \begin{pmatrix} 1 \\ 1 \\ 1 \end{pmatrix} + Z \begin{pmatrix} 0 \\ 0 \\ -I_f \end{pmatrix} \quad V = \begin{pmatrix} 0.52 - 0.025i \\ 0.464 - 0.028i \\ 0 \end{pmatrix} \quad \text{pu}$$

Branch voltage drop

$$V_b := C \cdot V$$

$$V_b = \begin{pmatrix} 0.056 + 2.801i \times 10^{-3} \\ 0.464 - 0.028i \\ 0.52 - 0.025i \\ 0.52 - 0.025i \\ 0.464 - 0.028i \end{pmatrix} \quad \text{pu}$$

Branch Current

$$I_b := y_{\text{prim}} \cdot V_b$$

$$I_b = \begin{pmatrix} -0.098 + 0.73i \\ 0.182 - 4.626i \\ 0.35 - 5.53i \\ -0.252 - 5.2i \\ -0.28 - 4.644i \end{pmatrix} \quad \text{pu}$$

Note :Sum branch 2 and branch 3 currents equals fault current