

## EE544 HW2

1. Refer to problem 1 HW 1

a. Now use the Ranade method

Assume the source impedance is  $j0.001$  pu.

Ignoring loads and converting the voltage source at Bus 1 to a current source calculate the admittance( $Y$ ) and impedance( $Z$ ) matrices.

Guess suitable values for  $v_2$  and  $v_3$

1. Compute load currents

2. Solve  $I = Y V$  for  $V$

3. set  $v_2$  and  $v_3$  to the values calculated in step 2 (  $v_1$  better be ??)

Repeat 1-3 to convergence to 3 decimal places.

b. Now use Kersting's 'ladder method' for radial systems

Assume  $v_1 = 1$  pu

1. Calculate the current from bus 2 to bus 3

2. Calculate  $v_2$


3. Calculate the current from bus 1 to bus 2

4. Calculate  $v_1$

5. Compare  $v_1$  with the specified value of  $v_1=1$ ; use the difference(error) to come up with a new guess  $v_3$

Repeat steps 1-5 until the calculate  $v_1 = 1$  to 3 decimal places.

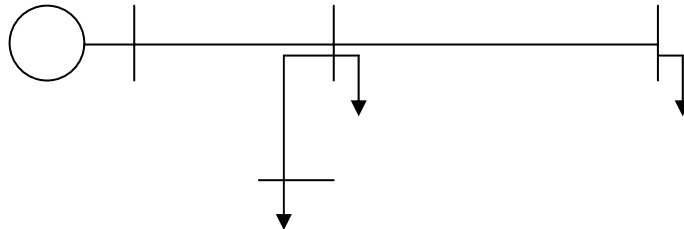c. How would you modify the ladder method for the system below?



The analysis of three-phase, unbalanced, systems will involve merely reinterpreting the impedances as  $3 \times 3$  or  $4 \times 4$  matrices and bus voltage and injected current as a 3- or 4- element vector.


2.5 A single-phase lateral serves four transformers as shown in Figure 2.15. Assume that each customer's maximum demand is  $15.5 \text{ kW} + j7.5 \text{ kVAr}$ . The impedance of the single-phase lateral is  $z = 0.4421 + j0.3213 \Omega/1,000 \text{ ft}$ . The four transformers are rated as:

T1 and T2: 37.5 kVA, 2,400–240 volts,  $Z = 0.01 + j0.03$  per unit

T3 and T4: 50 kVA, 2,400–240 volts,  $Z = 0.015 + j0.035$  per unit

Use the DFs found in Table 2.2 and determine:

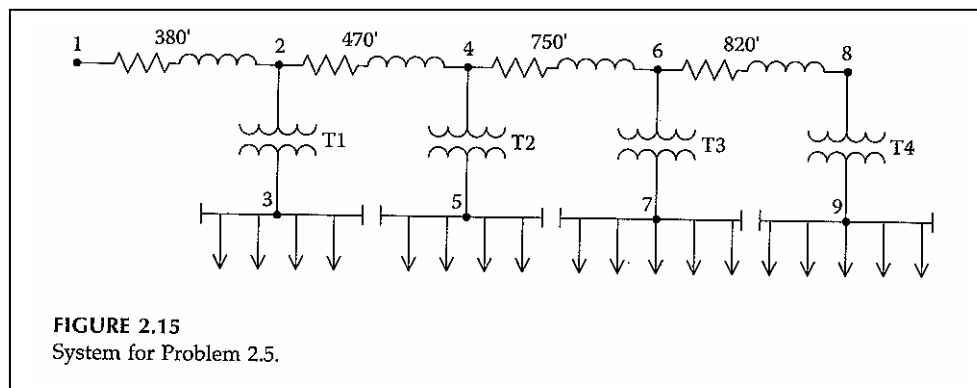1. The 15-minute maximum diversified kW and kVAr demands on each transformer
2. The 15-minute maximum diversified kW and kVAr demands for each line section
3. If the voltage at Node 1 is  $2,600/0$  volts, determine the voltage at nodes 2, 3, 4, 5, 6, 7, 8, and 9. In calculating the voltages, take into account diversity using the answers from 1 and 2 above.



6. Take the maximum diversified demand from node 1 to node 2 and allocate that out to each of the four transformers based upon their kVA ratings. To do this, take the maximum diversified demand and divide by 175 (total kVA of the four transformers). Now multiply each transformer kVA rating by that number to give how much of the total diversified demand is being served by each transformer. Again, calculate all of the voltages.