

Lecture 3

Text: Section 2.2-2.3

Key Ideas-- Power in single phase ac circuits

Instantaneous power $p(t)=v(t) i(t)$ always oscillates

The average power corresponds to useful work and is called real power P

Reactive power Q is a measure of the alternating part needed to charge and discharge inductors and capacitors in the ac cycle

Complex power is defined as $S=VI^*$ and equals $P+jQ$

Apparent power is $|S|=|V||I|$ volt-amperes and determines the 'size' of power equipment

Instantaneous power (See p.46-48)

If $v(t) = V_{max} \cos(\omega t + \beta) = \sqrt{2} |V| \cos(\omega t + \beta)$ and $i(t) = I_{max} \cos(\omega t + \delta) = \sqrt{2} |I| \cos(\omega t + \delta)$

$$p(t) = (1/2)V_{max} I_{max} [\cos(\delta - \beta) + \cos\{2(\omega t + \delta) - (\delta - \beta)\}]$$

$$p(t) = |V||I|\cos\phi [1 + \cos\{2(\omega t + \delta)\}] + |V||I|\sin\phi \sin\{2(\omega t + \delta)\}$$

Term 1

Term 2

Where $\phi = \delta - \beta$, the angle by which voltage leads the current, is called the "power factor angle"

Term 1 is oscillating power/energy with average value $P = VI\cos\phi$.

This term corresponds to net work done or energy provided. P is called real power measured in Watts

The second term is a sinusoidal or alternating component with amplitude $Q = VI \sin \phi$

but no AVERAGE value, work done, or net energy supply Q is called reactive power measured in VARS. Reactive power is the oscillating energy flow needed to charge/discharge inductors and capacitors in the ac cycle (See Exmple 2.1).

Complex power is defined as $S = VI^* = P + jQ$

Apparent power is $|S| = |V||I| = \sqrt{P^2 + Q^2}$ VA

Note $|I| = |S|/|V| = \sqrt{(P^2+Q^2)} / |V|$

Although Q does not provide any net energy the corresponding oscillating flow has to be maintained if we have L's and C's. The current required depends on P and Q. If you must support lots of Q the current will be high and you need bigger equipment.

Power factor $PF = \cos \phi = \cos(\delta - \beta) = \cos(\text{voltage phase} - \text{current phase})$

Need to tell if Lagging or leading

Resistor $PF = 1$ Inductor $PF = 0$ lag Capacitor $PF = 0$ lead


Power calculations $S = VI^*$ is the most convenient

Can use $P = |V||I|\cos\phi$. $Q = |V||I|\sin\phi$

H. For impedance Z with Voltage V across, or current I through can use

$S = |I|^2 Z = |V|^2 / Z^*$ watch the conjugate

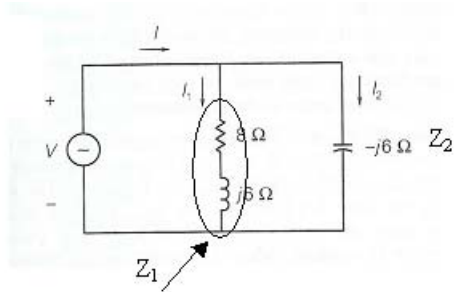Example Continued from Lecture 2-Power Calculations



$$I := 10 + 0i \quad \text{A}$$

$$Z_1 := 8 + 6i$$

$$Z_2 := -6i \quad \text{ohms}$$

The equivalent (parallel) impedance as viewed from the source is

$$Z := Z_1 \cdot \frac{Z_2}{Z_1 + Z_2} \quad Z = 4.5 - 6i \quad \text{ohms}$$

$$|Z| = 7.5 \quad \arg(Z) = -53.13 \text{ deg}$$


Thus

$$V := Z \cdot I \quad V = 45 - 60i \quad |V| = 75 \quad \arg(V) = -53.13 \text{ de}$$

$$I_1 := \frac{V}{Z_1} \quad I_1 = -7.5i \quad |I_1| = 7.5 \quad \arg(I_1) = -90 \text{ deg}$$

$$I_2 := \frac{V}{Z_2} \quad I_2 = 10 + 7.5i \quad |I_2| = 12.5 \quad \arg(I_2) = 36.87 \text{ deg}$$

Phasor Diagram

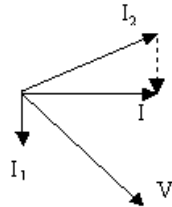

Complex Power

Delivered by source

$$S_s := V \cdot \bar{I} \quad S_s = 450 - 600i \quad \text{VA} \quad 450\text{W and } -600\text{Var}$$

Delivered to Z1

$$S_1 := V \cdot \bar{I}_1 \quad S_1 = 450 + 337.5i \quad \text{VA}$$

$$S_2 := V \cdot \bar{I}_2 \quad S_2 = -937.5i \quad \text{VA}$$

Complex Powers and power factor

At source

$$|S_s| = 750 \quad \text{VA}$$

$$\text{pfs} := \cos(\arg(V) - \arg(I)) \quad \text{pfs} = 0.6 \quad \text{Leading}$$

Load 1

$$|S_1| = 562.5 \quad \text{VA}$$


$$\text{pf1} := \cos(\arg(V) - \arg(I_1)) \quad \text{pf1} = 0.8 \quad \text{Lag}$$

Load 2

$$|S_2| = 937.5 \quad \text{VA}$$

$$\text{pf2} := \cos(\arg(V) - \arg(I_2)) \quad \text{pf2} = 0 \quad \text{Lead}$$

Complex Power Conservation

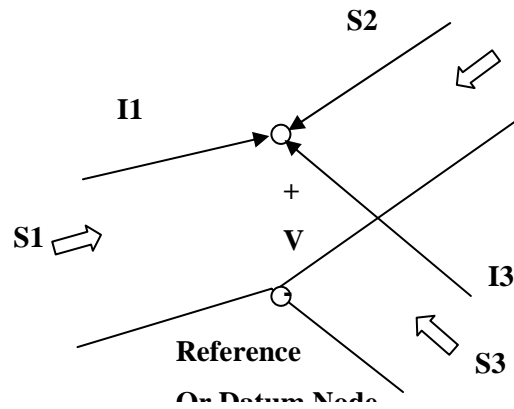

KCL $I_1 + I_2 + I_3 = 0 \Rightarrow V I_1^* + V I_2^* + V I_3^* = 0 \Rightarrow S_1 + S_2 + S_3 = 0$ Complex power conservation

Thus $P_1 + P_2 + P_3 = 0$

$Q_1 + Q_2 + Q_3 = 0$

This Mathcad example explores the time variation of instantaneous power. We will look at a pair of voltage and current with different phase relationships and show plots of instantaneous power as well as the values of corresponding real power reactive power and power factor.

Frequency $\omega := 377$

When plotting in Mathcad we must specify the range of the independent variable and the sample instants for plotting. We will plot zero to 0.05 second, 3 cycles of 60 Hz, at 0.1 ms intervals.

Time range for plotting points every .1 mS $t := 0, .0001.. .05$

Resistive Load

Let $v_L(t) := \sqrt{2} \cdot 1 \cdot \cos(\omega \cdot t)$ $V_L := 1 \cdot e^{j \cdot 0 \text{deg}}$ $i_L(t) := \sqrt{2} \cdot 1 \cdot \cos(\omega \cdot t)$ $I_L := 1 \cdot e^{j \cdot 0 \text{deg}}$

$\underline{V}_L := 1 \cdot e^{j \cdot 0 \text{deg}}$ $|V_L| = 1$ $\delta := \arg(V_L)$ $\delta = 0 \text{deg}$

$\underline{I}_L := 1 \cdot e^{j \cdot 0 \text{deg}}$ $|I_L| = 1$ $\beta := \arg(I_L)$ $\beta = 0 \text{deg}$

$\phi := \delta - \beta$ $\phi = 0$


Instantaneous power

Directly $p(t) := 2 \cdot \cos(\omega \cdot t)^2$

Book formula

$\underline{p}(t) := |V_L| \cdot |I_L| \cdot \cos(\phi) \cdot [1 + \cos[2 \cdot (\omega \cdot t + \delta)]] + |V_L| \cdot |I_L| \cdot \cos(\phi) \cdot \sin[2 \cdot (\omega \cdot t + \delta)]$

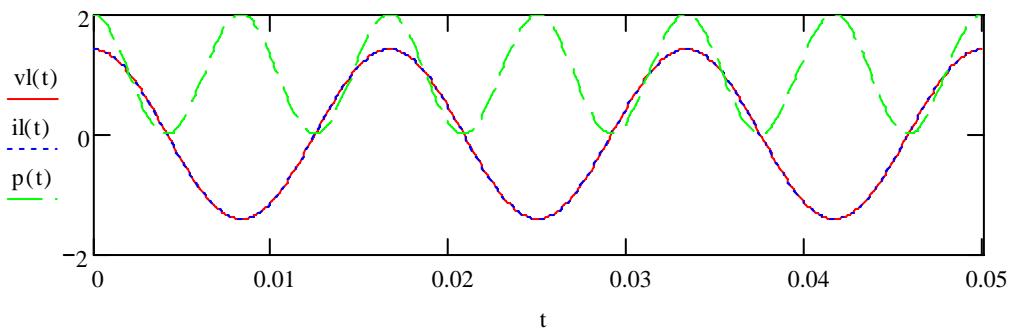Mathcad $\underline{p}(t) := v_L(t) \cdot i_L(t)$



Note $p(t)$ oscillates with double frequency and average value of 1; The flow of energy is unidirectional. So we have an oscillation but only real power transfer

Complex power $\underline{S} := V_L \cdot \overline{I_L}$ $S = 1$ VA $P := 1$ W $Q := 0$ VAR

Power Factor $PF := \cos(\phi)$ $PF = 1$

Capacitor Load

$$v_L(t) := \sqrt{2} \cdot 1 \cdot \cos(\omega \cdot t) \qquad i_L(t) := \sqrt{2} \cdot 1 \cdot \cos(\omega \cdot t + 90\text{deg})$$

$$\underline{V}_L := 1 \cdot e^{j \cdot 0\text{deg}} \quad |V_L| = 1 \quad \delta := \arg(V_L) \quad \delta = 0\text{deg}$$

$$\underline{I}_L := 1 \cdot e^{j \cdot 90\text{deg}} \quad |I_L| = 1 \quad \beta := \arg(I_L) \quad \beta = 90\text{deg}$$


$$\phi := \delta - \beta \qquad \phi = -90\text{deg}$$

Instantaneous power

Book formula

$$p(t) := |V_L| \cdot |I_L| \cdot \cos(\phi) \cdot [1 + \cos[2 \cdot (\omega \cdot t + \delta)]] + |V_L| \cdot |I_L| \cdot \cos(\phi) \cdot \sin[2 \cdot (\omega \cdot t + \delta)]$$

Mathcad $p(t) := v_L(t) \cdot i_L(t)$

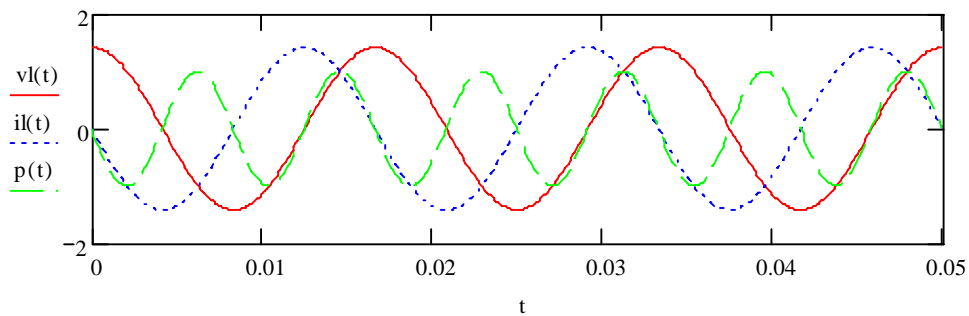

Note $p(t)$ oscillates with double frequency and average value of 0; The flow of energy is alternating with zero net energy. As Voltage goes down, capacitor discharges and release energy back into the source. Power flow is negative. Then as voltage decrease and goes more negative, capacitor charges in the negative direction and takes and stores energy from the source. Power and energy flow into the capacitor...

Complex power

$$\underline{S} := V_L \cdot \overline{I}_L \qquad S = -i \quad \text{VA} \quad P := 0 \quad \text{W} \quad Q := -1 \quad \text{VAR}$$

Power Factor

$$\text{PF} := \cos(\phi) \qquad \text{PF} = 0 \quad \text{lead}$$

Inductor Load

$$v_L(t) := \sqrt{2} \cdot 1 \cdot \cos(\omega \cdot t) \quad V_L := 1 \cdot e^{j \cdot 0 \text{deg}} \quad i_L(t) := \sqrt{2} \cdot 1 \cdot \cos((\omega \cdot t - 90 \text{deg})) \quad I_L := 1 \cdot e^{j \cdot -90 \text{deg}}$$

$$V_L := 1 \cdot e^{j \cdot 0 \text{deg}} \quad |V_L| = 1 \quad \delta := \arg(V_L) \quad \delta = 0 \text{deg}$$

$$I_L := 1 \cdot e^{j \cdot -90 \text{deg}} \quad |I_L| = 1 \quad \beta := \arg(I_L) \quad \beta = -90 \text{deg}$$


$$\phi := \delta - \beta \quad \phi = 1.571 \quad \text{Voltage leads current}$$

Instantaneous power

Book formula

$$p(t) := |V_L| \cdot |I_L| \cdot \cos(\phi) \cdot [1 + \cos[2 \cdot (\omega \cdot t + \delta)]] + |V_L| \cdot |I_L| \cdot \cos(\phi) \cdot \sin[2 \cdot (\omega \cdot t + \delta)]$$

Mathcad $p(t) := v_L(t) \cdot i_L(t)$

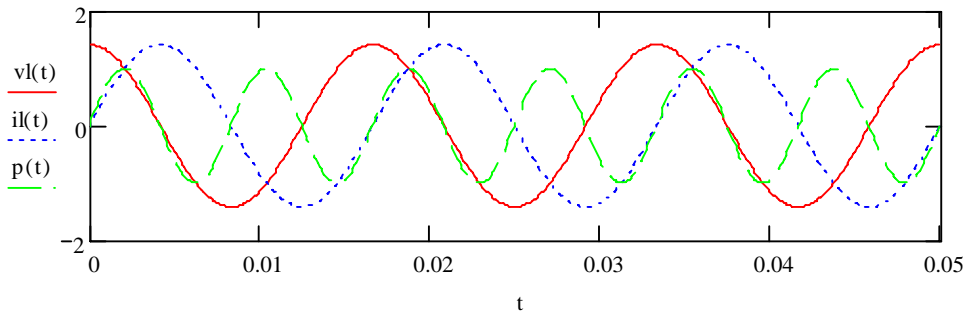

Note $p(t)$ oscillates with double frequency and average value of 0; The flow of energy is alternating with zero net energy. As current goes up, so does the magnetic field and energy stored in the inductor. Power and Energy flow is positive. Then as current decreases and energy is released and power flows back to the source

Complex power $S := V_L \cdot \bar{I}_L \quad S = i \quad \text{VA} \quad P := 0 \quad W \quad Q := 1 \quad \text{VAR}$

Power Factor

$$PF := \cos(\phi) \quad PF = 0 \quad \text{lag}$$

General case

$$v(t) := \sqrt{2} \cdot 1 \cdot \cos(\omega \cdot t)$$

$$i(t) := \sqrt{2} \cdot 1 \cdot \cos(\omega \cdot t - 30\text{deg})$$

$$V_L := 1 \cdot e^{j \cdot 0\text{deg}}$$

$$I_L := 1 \cdot e^{j \cdot -30\text{deg}}$$

$$|V_L| = 1 \quad \delta := \arg(V_L) \quad \delta = 0\text{deg}$$


$$|I_L| = 1 \quad \beta := \arg(I_L) \quad \beta = -30\text{deg}$$

$$\phi := \delta - \beta \quad \phi = 30\text{deg}$$

Instantaneous power

Book formula

$$p(t) := |V_L| \cdot |I_L| \cdot \cos(\phi) \cdot [1 + \cos[2 \cdot (\omega \cdot t + \delta)] + |V_L| \cdot |I_L| \cdot \cos(\phi) \cdot \sin[2 \cdot (\omega \cdot t + \delta)]]$$

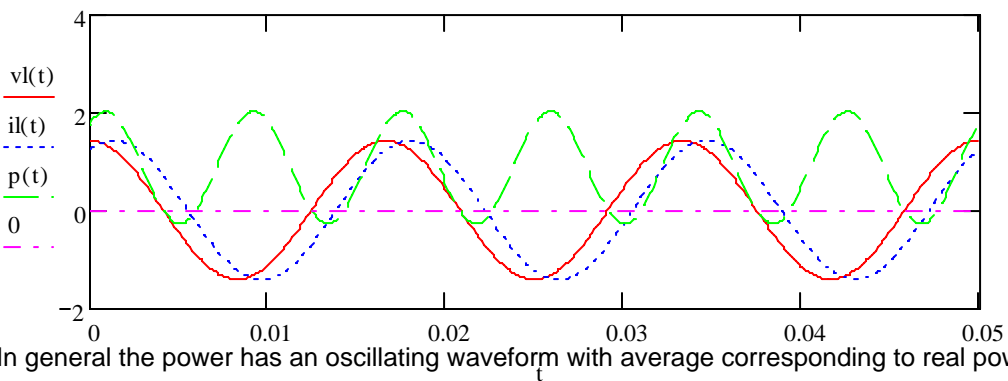

In general the power has an oscillating waveform with average corresponding to real power

Complex power $S := V_L \cdot \overline{I_L} \quad S = 0.866 + 0.5i \quad \text{VA} \quad P := 0.866 \quad \text{W} \quad Q := .5 \quad \text{VAR}$

Power Factor $PF := \cos(\phi) \quad PF = 0.866 \quad \text{lag}$