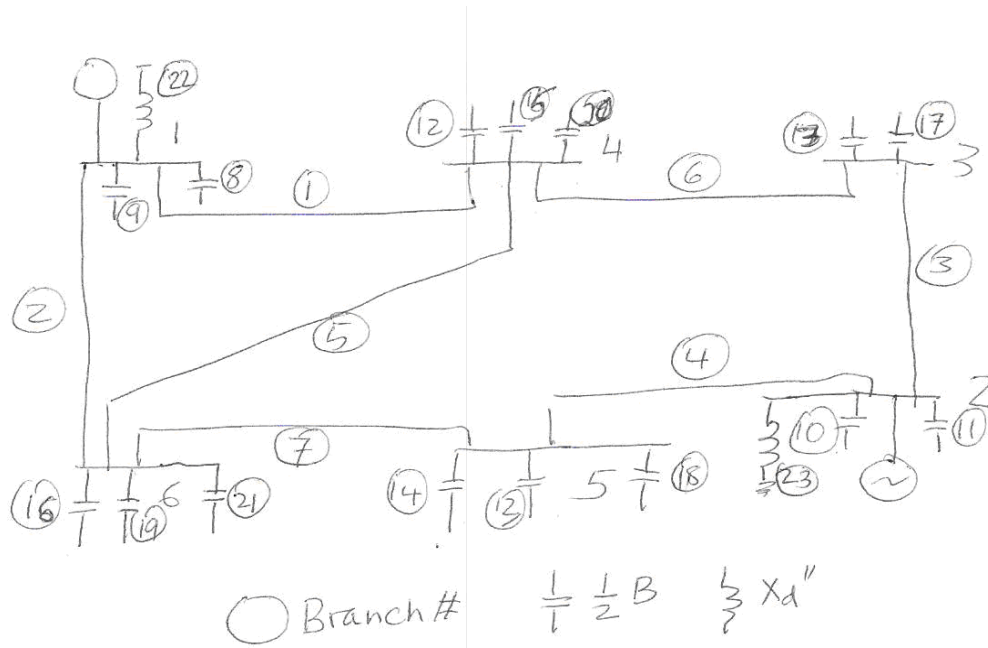


The system can be modeled as 23 branches-- 7 lines, fourteen shunts (Pi model, half shunt admittance at each end) and 2 generator subtransient impedances to ground.



Too lazy to type 23x23 matrix. I will set up vectors with to and from buses for each branch and then use a loop to build connection matrix. Later these will lead to 'linked-lists' for sparse operations

$$\text{From} := (1 \ 1 \ 2 \ 2 \ 4 \ 3 \ 5 \ 1 \ 1 \ 2 \ 2 \ 4 \ 3 \ 5 \ 4 \ 6 \ 3 \ 5 \ 6 \ 4 \ 6 \ 1 \ 2)^T$$

$$\text{To} := (4 \ 6 \ 3 \ 5 \ 6 \ 4 \ 6 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0 \ 0)^T$$

zero out C matrix

$i := 1, 2 \dots 23$ $j := 1, 2 \dots 6$ $C_{i,j} := 0$

Build C using From and To lists

$j := 1, 2 \dots 23$ $C_{j, \text{From}_j} := 1$

$j := 1, 2 \dots 7$ $C_{j, \text{To}_j} := \begin{cases} 0 & \text{if } \text{To}_j = 0 \\ -1 & \text{otherwise} \end{cases}$

C =

	1	2	3	4	5	6
1	1	0	0	-1	0	0
2	1	0	0	0	0	-1
3	0	1	-1	0	0	0
4	0	1	0	0	-1	0
5	0	0	0	1	0	-1
6	0	0	1	-1	0	0
7	0	0	0	0	1	-1
8	1	0	0	0	0	0
9	1	0	0	0	0	0
10	0	1	0	0	0	0
11	0	1	0	0	0	0
12	0	0	0	1	0	0
13	0	0	1	0	0	0
14	0	0	0	0	1	0
15	0	0	0	1	0	0
16	0	0	0	0	0	1
17	0	0	1	0	0	0
18	0	0	0	0	1	0
19	0	0	0	0	0	1
20	0	0	0	1	0	0
21	0	0	0	0	0	1
22	1	0	0	0	0	0
23	0	1	0	0	0	0

Primitive admittance matrix for 23 branches

$$m := 1, 2 \dots 23 \quad n := 1, 2 \dots 23 \quad y_{m,n} := 0$$

Line series impedance

$$y_{1,1} := \frac{1}{.02 + .185i} \quad y_{2,2} := \frac{1}{.031 + .259i} \quad y_{3,3} := \frac{1}{.006 + .025i}$$

$$y_{4,4} := \frac{1}{.071 + .32i} \quad y_{5,5} := \frac{1}{.024 + .204i} \quad y_{6,6} := \frac{1}{.075 + .067i}$$

$$y_{7,7} := \frac{1}{.025 + .15i}$$

Half of line shunt admittance, one at each terminal bus for the line

$$y_{8,8} := \frac{.009i}{2} \quad y_{9,9} := \frac{.01i}{2} \quad y_{10,10} := 0$$

$$y_{11,11} := \frac{.015i}{2} \quad y_{12,12} := \frac{.01i}{2} \quad y_{13,13} := 0 \quad y_{14,14} := \frac{.017i}{2}$$

Generator subtransient

$$y_{22,22} := \frac{1}{.1i} \quad y_{23,23} := \frac{1}{.1i}$$

$$m := 15, 16 \dots 21 \quad y_{m,m} := y_{m-7, m-7} \quad \text{Repeat other half of susceptance}$$

Compute admittance Matrix

$$Y := C^T \cdot y \cdot C$$

$$\text{Re}(Y) = \begin{pmatrix} 1.033 & 0 & 0 & -0.578 & 0 & -0.456 \\ 0 & 9.738 & -9.077 & 0 & -0.661 & 0 \\ 0 & -9.077 & 16.493 & -7.415 & 0 & 0 \\ -0.578 & 0 & -7.415 & 8.562 & 0 & -0.569 \\ 0 & -0.661 & 0 & 0 & 1.742 & -1.081 \\ -0.456 & 0 & 0 & -0.569 & -1.081 & 2.106 \end{pmatrix}$$

$$\text{Im}(Y) = \begin{pmatrix} -19.14 & 0 & 0 & 5.343 & 0 & 3.806 \\ 0 & -50.792 & 37.821 & 0 & 2.978 & 0 \\ 0 & 37.821 & -44.446 & 6.624 & 0 & 0 \\ 5.343 & 0 & 6.624 & -16.793 & 0 & 4.835 \\ 0 & 2.978 & 0 & 0 & -9.449 & 6.486 \\ 3.806 & 0 & 0 & 4.835 & 6.486 & -15.109 \end{pmatrix}$$

Using Rules

In the PDF the right half of the matrix will appear on the last page

$$YR := \begin{pmatrix} y_{1,1} + y_{2,2} + y_{8,8} + y_{9,9} + y_{22,22} & 0 & 0 \\ 0 & y_{3,3} + y_{4,4} + y_{23,23} + y_{10,10} + y_{11,11} & -y_{3,} \\ 0 & -y_{3,3} & y_{3,3} + y_{6,6} + y_1 \\ -y_{1,1} & 0 & -y_{6,} \\ 0 & -y_{4,4} & 0 \\ -y_{2,2} & 0 & 0 \end{pmatrix}$$

$$\text{Re}(YR) = \begin{pmatrix} 1.033 & 0 & 0 & -0.578 & 0 & -0.456 \\ 0 & 9.738 & -9.077 & 0 & -0.661 & 0 \\ 0 & -9.077 & 16.493 & -7.415 & 0 & 0 \\ -0.578 & 0 & -7.415 & 8.562 & 0 & -0.569 \\ 0 & -0.661 & 0 & 0 & 1.742 & -1.081 \\ -0.456 & 0 & 0 & -0.569 & -1.081 & 2.106 \end{pmatrix}$$

$$\text{Im}(YR) = \begin{pmatrix} -19.14 & 0 & 0 & 5.343 & 0 & 3.806 \\ 0 & -50.792 & 37.821 & 0 & 2.978 & 0 \\ 0 & 37.821 & -44.446 & 6.624 & 0 & 0 \\ 5.343 & 0 & 6.624 & -16.793 & 0 & 4.835 \\ 0 & 2.978 & 0 & 0 & -9.449 & 6.486 \\ 3.806 & 0 & 0 & 4.835 & 6.486 & -15.109 \end{pmatrix}$$

Comparing the two they are the same, with slight differences in the 3rd decimal place(Why??)

Trying to automate the construction of Y in Mathcad is a little clumsy, since I took the array origin as 1.

First I will define the reference (usually node 0) as node 7. Then I will use the rules to build a 7x7 matrix. Finally I will throw away row and column 7

$$\text{From} := (1 \ 1 \ 2 \ 2 \ 4 \ 3 \ 5 \ 1 \ 1 \ 2 \ 2 \ 4 \ 5 \ 4 \ 6 \ 3 \ 5 \ 4 \ 6 \ 4 \ 6 \ 1 \ 2)^T$$

$$\text{To} := (4 \ 6 \ 3 \ 5 \ 6 \ 4 \ 6 \ 7 \ 7 \ 7 \ 7 \ 7 \ 7 \ 7 \ 7 \ 7 \ 7 \ 7 \ 7 \ 7 \ 7 \ 7 \ 7 \ 7)^T$$

$$m := 1, 2 \dots 7 \quad n := 1, 2 \dots 7 \quad Y7_{m,n} := 0$$

$$m := 1, 2 \dots 23$$

$$Y7_{\text{From}_m, \text{From}_m} := Y7_{\text{From}_m, \text{From}_m} + y_{m,m}$$

$$Y7_{\text{To}_m, \text{To}_m} := Y7_{\text{To}_m, \text{To}_m} + y_{m,m}$$

$$Y7_{\text{From}_m, \text{To}_m} := Y7_{\text{From}_m, \text{To}_m} - y_{m,m}$$

$$Y7_{\text{To}_m, \text{From}_m} := Y7_{\text{To}_m, \text{From}_m} - y_{m,m}$$

$$\underline{\underline{Y}} := \text{submatrix}(Y7, 1, 6, 1, 6)$$

$$\text{Re}(Y) = \begin{pmatrix} 1.033 & 0 & 0 & -0.578 & 0 & -0.456 \\ 0 & 9.738 & -9.077 & 0 & -0.661 & 0 \\ 0 & -9.077 & 16.493 & -7.415 & 0 & 0 \\ -0.578 & 0 & -7.415 & 8.562 & 0 & -0.569 \\ 0 & -0.661 & 0 & 0 & 1.742 & -1.081 \\ -0.456 & 0 & 0 & -0.569 & -1.081 & 2.106 \end{pmatrix}$$

$$\text{Im}(Y) = \begin{pmatrix} -19.14 & 0 & 0 & 5.343 & 0 & 3.806 \\ 0 & -50.792 & 37.821 & 0 & 2.978 & 0 \\ 0 & 37.821 & -44.441 & 6.624 & 0 & 0 \\ 5.343 & 0 & 6.624 & -16.781 & 0 & 4.835 \\ 0 & 2.978 & 0 & 0 & -9.465 & 6.486 \\ 3.806 & 0 & 0 & 4.835 & 6.486 & -15.11 \end{pmatrix}$$

Coupled case

with coupling

coupling impedance

admittance

$$z_c := \begin{pmatrix} .071 + .32i & .03i \\ .03i & .025 + .15i \end{pmatrix} \quad y_c := z_c^{-1} \quad y_c = \begin{pmatrix} 0.693 - 3.024i & -0.233 + 0.566i \\ -0.233 + 0.566i & 1.145 - 6.589i \end{pmatrix}$$

The following terms in the branch primitive admittance will change

Branch 2-5 is #4 and branch 2-6 is #7

$$y_{4,4} := y_{c1,1} \quad y_{4,7} := y_{c1,2} \quad y_{7,4} := y_{c2,1} \quad y_{7,7} := y_{c2,2} \quad y_{4,4} = 0.693 - 3.024i$$

$$Y_M := C^T \cdot y \cdot C$$

$$\text{Re}(Y_M) = \begin{pmatrix} 1.033 & 0 & 0 & -0.578 & 0 & -0.456 \\ 0 & 9.77 & -9.077 & 0 & -0.926 & 0.233 \\ 0 & -9.077 & 16.493 & -7.415 & 0 & 0 \\ -0.578 & 0 & -7.415 & 8.562 & 0 & -0.569 \\ 0 & -0.926 & 0 & 0 & 2.303 & -1.378 \\ -0.456 & 0.233 & 0 & -0.569 & -1.378 & 2.169 \end{pmatrix}$$

$$\text{Im(YM)} = \begin{pmatrix} -19.14 & 0 & 0 & 5.343 & 0 & 3.806 \\ 0 & -50.838 & 37.821 & 0 & 3.59 & -0.566 \\ 0 & 37.821 & -44.446 & 6.624 & 0 & 0 \\ 5.343 & 0 & 6.624 & -16.793 & 0 & 4.835 \\ 0 & 3.59 & 0 & 0 & -10.73 & 7.155 \\ 3.806 & -0.566 & 0 & 4.835 & 7.155 & -15.212 \end{pmatrix}$$

Using rules

Set admittance parameter for line 2-5 and 5-6 to zero and build Y as usual

$$\begin{aligned} y_{4,7} &:= 0 & y_{7,4} &:= 0 \\ m := 1, 2 \dots 7 \quad n := 1, 2 \dots 7 & \quad Y_{m,n} &:= 0 \\ m := 1, 2 \dots 23 \\ Y_{\text{From}_m, \text{From}_m} &:= Y_{7, \text{From}_m, \text{From}_m} + y_{m,m} \\ Y_{\text{To}_m, \text{To}_m} &:= Y_{7, \text{To}_m, \text{To}_m} + y_{m,m} \\ Y_{\text{From}_m, \text{To}_m} &:= Y_{7, \text{From}_m, \text{To}_m} - y_{m,m} \\ Y_{\text{To}_m, \text{From}_m} &:= Y_{7, \text{To}_m, \text{From}_m} - y_{m,m} \\ \text{YMR} &:= \text{submatrix}(Y7, 1, 6, 1, 6) \end{aligned}$$

Now put in coupled branches using modified rules. In terms of class note
i=2 j= 5 k= 5 l=6

$$m := y_{c_{1,2}}$$

$$\text{YMR}_{2,5} := \text{YMR}_{2,5} + m \quad \text{YMR}_{5,2} := \text{YMR}_{5,2} + m$$

$$\text{YMR}_{6,5} := \text{YMR}_{6,5} + m \quad \text{YMR}_{5,6} := \text{YMR}_{5,6} + m$$

$$\text{YMR}_{6,2} := \text{YMR}_{6,2} - m \quad \text{YMR}_{2,6} := \text{YMR}_{2,6} - m$$

$$\text{YMR}_{5,5} := \text{YMR}_{5,5} - m \quad \text{YMR}_{5,5} := \text{YMR}_{5,5} - m$$

$$\text{Re(YMR)} = \begin{pmatrix} 1.033 & 0 & 0 & -0.578 & 0 & -0.456 \\ 0 & 9.77 & -9.077 & 0 & -0.926 & 0.233 \\ 0 & -9.077 & 16.493 & -7.415 & 0 & 0 \\ -0.578 & 0 & -7.415 & 8.562 & 0 & -0.569 \\ 0 & -0.926 & 0 & 0 & 2.303 & -1.378 \\ -0.456 & 0.233 & 0 & -0.569 & -1.378 & 2.169 \end{pmatrix}$$

$$\text{Re(YM)} = \begin{pmatrix} 1.033 & 0 & 0 & -0.578 & 0 & -0.456 \\ 0 & 9.77 & -9.077 & 0 & -0.926 & 0.233 \\ 0 & -9.077 & 16.493 & -7.415 & 0 & 0 \\ -0.578 & 0 & -7.415 & 8.562 & 0 & -0.569 \\ 0 & -0.926 & 0 & 0 & 2.303 & -1.378 \\ -0.456 & 0.233 & 0 & -0.569 & -1.378 & 2.169 \end{pmatrix}$$

$$\text{Im(YM)} = \begin{pmatrix} -19.14 & 0 & 0 & 5.343 & 0 & 3.806 \\ 0 & -50.838 & 37.821 & 0 & 3.59 & -0.566 \\ 0 & 37.821 & -44.446 & 6.624 & 0 & 0 \\ 5.343 & 0 & 6.624 & -16.793 & 0 & 4.835 \\ 0 & 3.59 & 0 & 0 & -10.73 & 7.155 \\ 3.806 & -0.566 & 0 & 4.835 & 7.155 & -15.212 \end{pmatrix}$$

$$\text{Im(YMR)} = \begin{pmatrix} -19.14 & 0 & 0 & 5.343 & 0 & 3.806 \\ 0 & -50.838 & 37.821 & 0 & 3.59 & -0.566 \\ 0 & 37.821 & -44.441 & 6.624 & 0 & 0 \\ 5.343 & 0 & 6.624 & -16.781 & 0 & 4.835 \\ 0 & 3.59 & 0 & 0 & -10.746 & 7.155 \\ 3.806 & -0.566 & 0 & 4.835 & 7.155 & -15.213 \end{pmatrix}$$

These match

Fault at bus 5

Uncoupled case $Z := Y^{-1}$ Bus Impedance Matrix

Three phase fault at bus 5 Assume pre-fault voltages of 1 pu

$$I_f'' := \frac{1}{Z_{5,5}} \quad I_f'' = 0.667 - 4.854i \quad \text{Fault current}$$

$$i := 1, 2 \dots 6 \quad V_i := 1 - \frac{Z_{i,5}}{Z_{5,5}} I_f''$$

$$V_i = \begin{pmatrix} 0.788 - 0.02i \\ 0.725 - 0.047i \\ 0.71 - 0.047i \\ 0.662 - 0.013i \\ 0 \\ 0.408 - 0.017i \end{pmatrix} \quad \text{Voltages}$$

$$I_b := y \cdot C \cdot V \quad i := 1, 2 \dots 7$$

$ I_{b_i} =$	From _i =	To _i =
0.675	1	4
1.456	1	6
0.578	2	3
2.253	2	5
1.239	4	6
0.576	3	4
2.73	5	6

$ I_{b_i} =$	From _i =	To _i =
7.88	1	7
7.261	2	7

Coupled case

$$\underline{Z} := \underline{Y}M^{-1}$$

Bus Impedance Matrix

Three phase fault at bus 5 Assume pre-fault voltages of 1 pu

$$\underline{I}_f' := \frac{1}{\underline{Z}_{5,5}}$$

$$I_f' = 0.776 - 5.209i \quad \text{Fault current}$$

$$i := 1, 2..6 \quad V_i := 1 - \frac{Z_{i,5}}{Z_{5,5}}$$

$$V_i = \begin{pmatrix} 0.772 - 0.024i \\ 0.703 - 0.054i \\ 0.688 - 0.054i \\ 0.637 - 0.019i \\ 0 \\ 0.365 - 0.026i \end{pmatrix}$$

Volatages

$$IbM := y \cdot C \cdot V \quad i := 1, 2..7$$

$$|IbM_i| =$$

$$From_i =$$

$$To_i =$$

0.726
1.56
0.607
2.188
1.325
0.607
2.45

1
1
2
2
4
3
5

4
6
3
5
6
4
6

$$i := 22, 23..23$$

$$|IbM_i| =$$

$$From_i =$$

$$To_i =$$

7.729
7.052

1
2

7
7

Compare

$i := 1, 2 \dots 7$	$ IbM_i =$	$ Ib_i =$	From _{i} =	To _{i} =
	0.726	0.675	1	4
	1.56	1.456	1	6
	0.607	0.578	2	3
	2.188	2.253	2	5
	1.325	1.239	4	6
	0.607	0.576	3	4
	2.45	2.73	5	6

Big difference in Line 5-6 which is coupled & close to fault!

	$-y_{1,1}$	0
3	0	$-y_{4,4}$
$0, 10 + y_{13,13}$	$-y_{6,6}$	0
6	$y_{1,1} + y_{6,6} + y_{5,5} + y_{8,8} + y_{12,12} + y_{13,13}$	0
	0	$y_{4,4} + y_{7,7} + y_{11,11} + y_{14,14}$
	$-y_{5,5}$	$-y_{7,7}$ $y_{2,2} + y_{5,5}$

$$\left. \begin{array}{l} -y_{2,2} \\ 0 \\ 0 \\ -y_{5,5} \\ -y_{7,7} \\ ,5 + y_{7,7} + y_{9,9} + y_{12,12} + y_{14,14} \end{array} \right)$$