


- For the boost converter that you analyzed in HW 2, develop a state space averaged model. The model should relate output voltage to Input voltage and duty cycle. Assume the following parameters from HW 2

$$E=100 \text{ V} \quad V_o= 125 \text{ V}$$

$$f = 5 \text{ kHz} \quad C= 500 \text{ uF} \quad L = 30 \text{ mH} \quad \text{Inductor resistance } R= 0.1 \text{ ohm}$$


Use Matlab to plot the step response of ouput voltage due to a change in duty cycle.

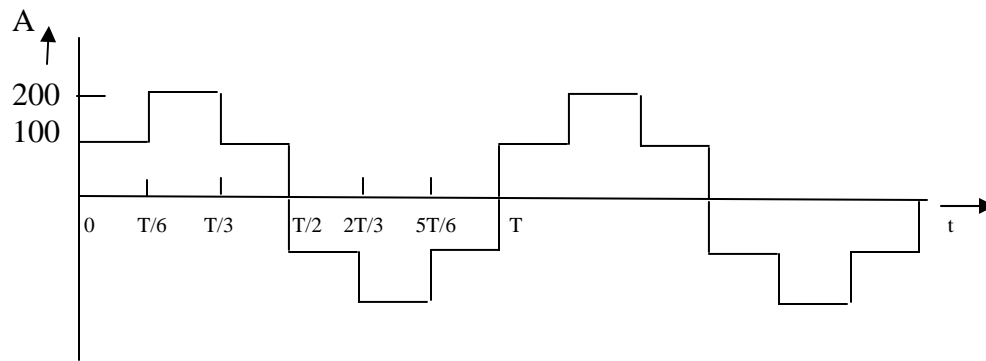- Find the Fourier Series for the current waveform shown below




Calculate the coefficients of the Fourier series and plot the line spectrum. Tell me which harmonics are zero.

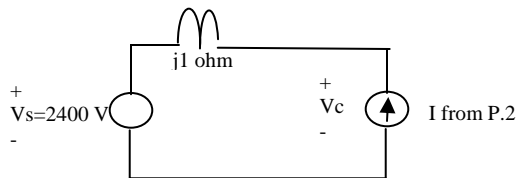- A converter injects the above current into a power system. On a per phase basis the power system can be represented by a 2400V, 60 Hz source with a short circuit(Thevenin) impedance of $j 1 \text{ ohm}$ as shown below:



- From the Fourier series for current in P.2 Determine the Fourier series for voltage V_c at the converter terminals and plot this voltage as a function of time. Calculate the THD
- Design a shunt filter shown below with the resonant frequency set at $10.6 \times 60 \text{ Hz}$, just below the 11^{th} Harmonic. Assume $R=100 \text{ ohm}$. Plot the

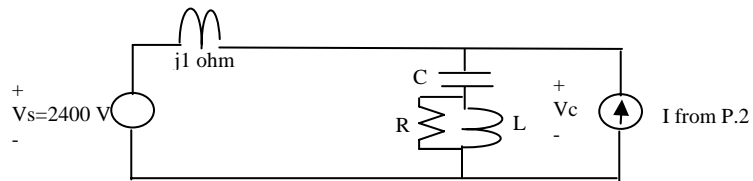impedance of the filter as a function of frequency. If you don't like the response, change R. Repeat part a.



Mandatory for Graduate Students/ Optional for others

4. For the waveform below determine parameters a, b and c so that the 3rd harmonic is zero.

